

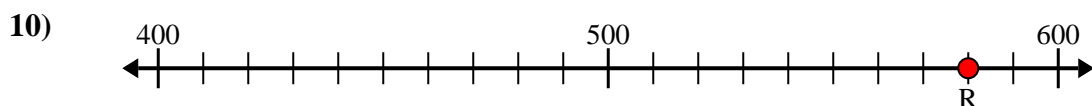
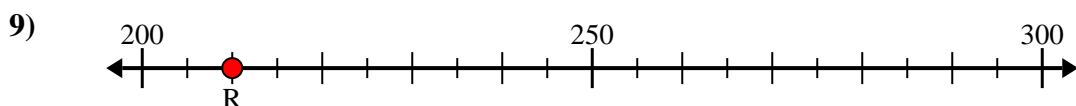
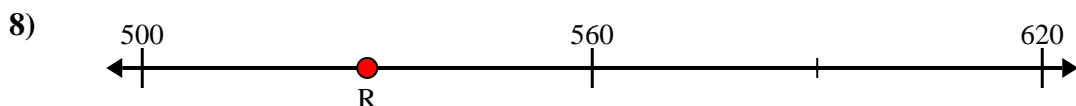
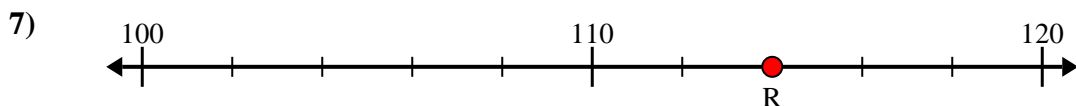
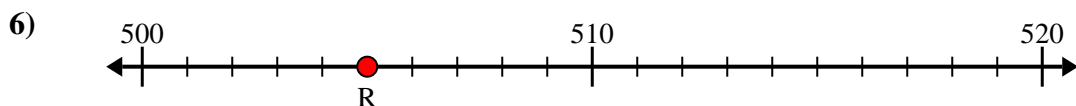
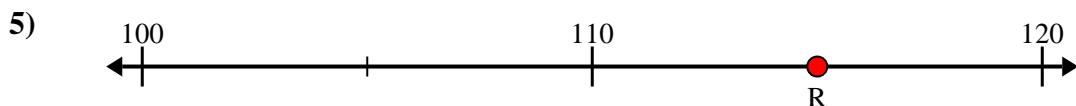
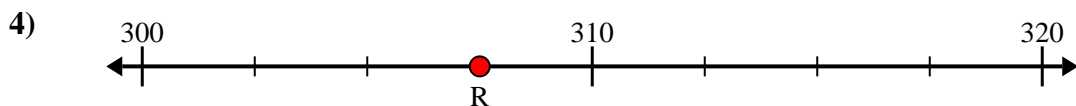
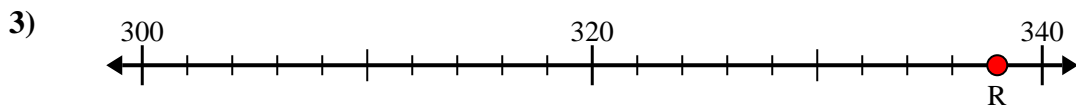


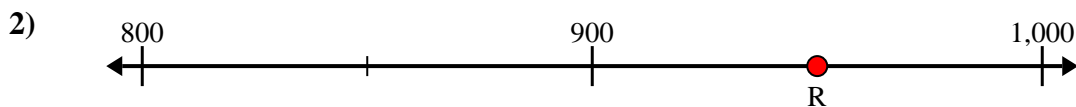

Find the value of R.

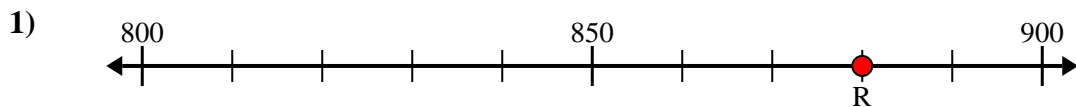

Answers

1. \_\_\_\_\_

2. \_\_\_\_\_

3. \_\_\_\_\_

4. \_\_\_\_\_

5. \_\_\_\_\_

6. \_\_\_\_\_

7. \_\_\_\_\_











8. \_\_\_\_\_

9. \_\_\_\_\_

10. \_\_\_\_\_



Find the value of R.

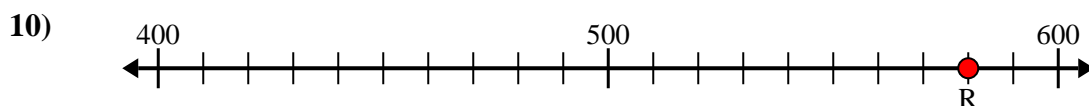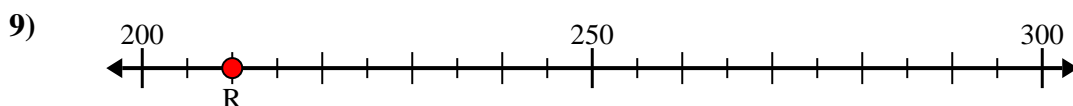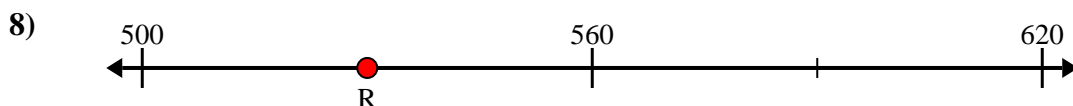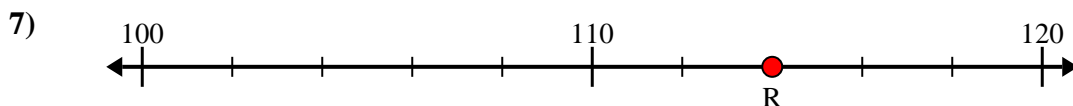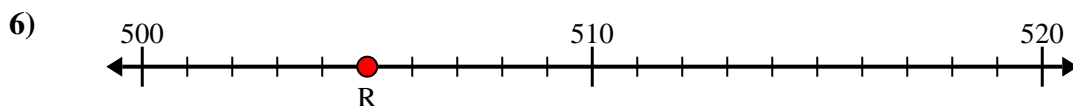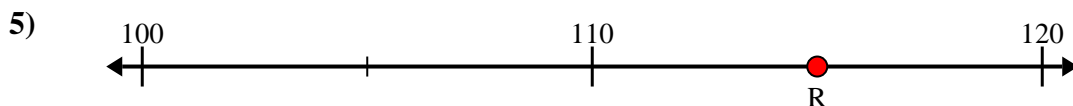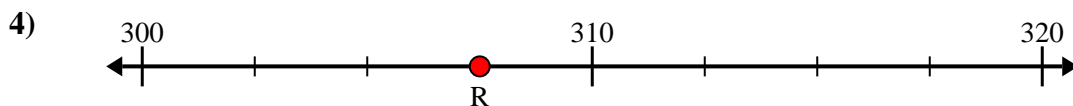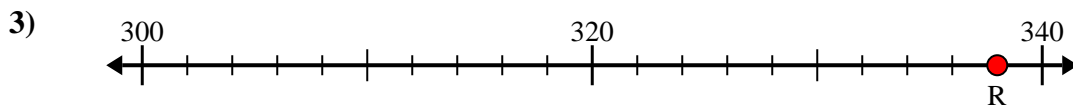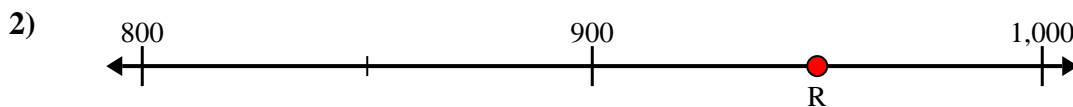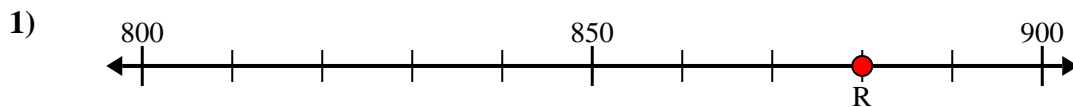

Answers

1. 880

2. 950

3. 338

4. 307.5

5. 115

6. 505

7. 114

8. 530

9. 210

10. 580