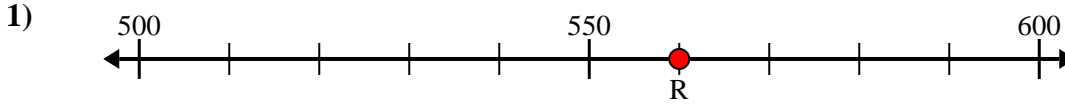





Find the value of R.


Answers




1. _____

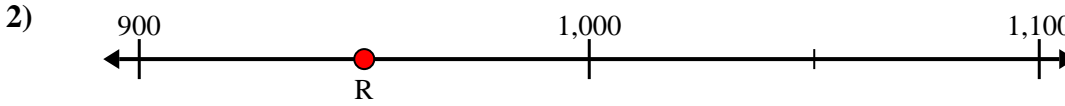


2. _____

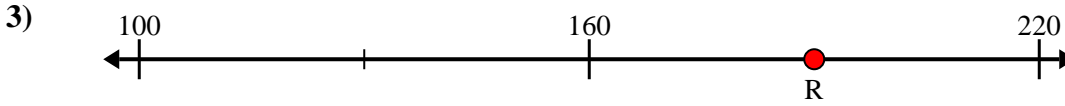


3. _____

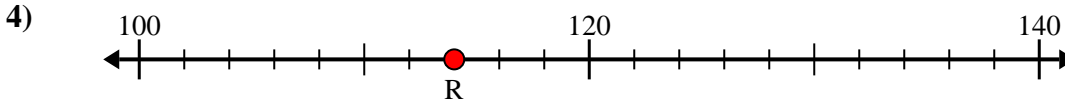


4. _____

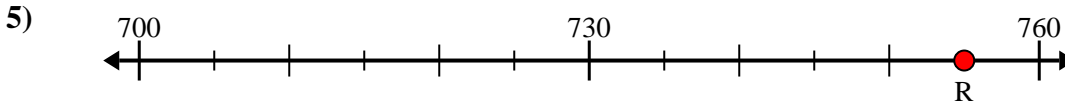


5. _____

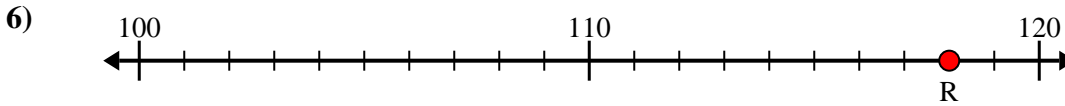


6. _____

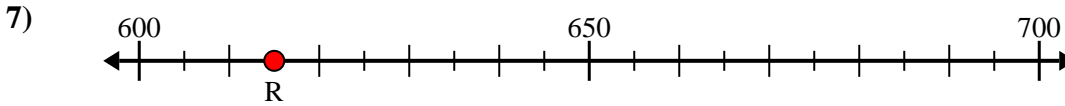


7. _____

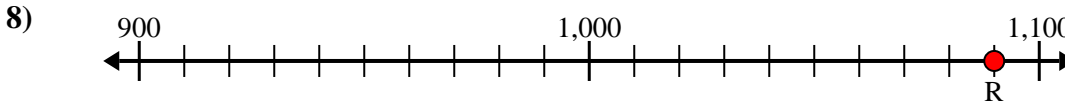

8. _____

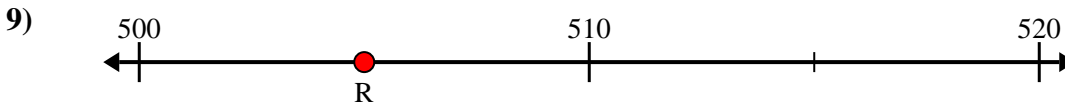











9. _____

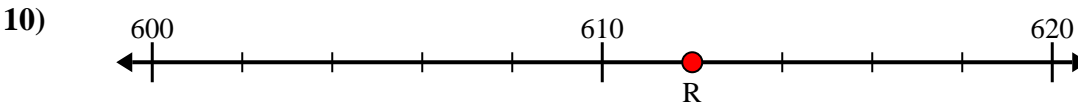

10. _____



Find the value of R.

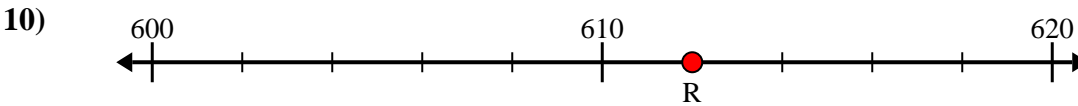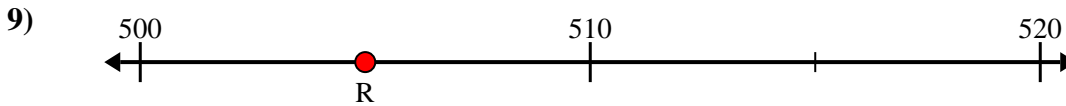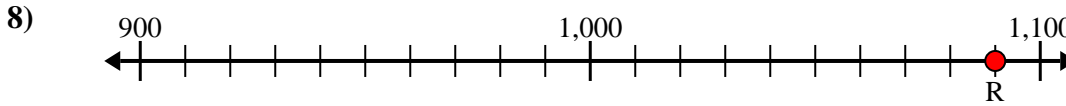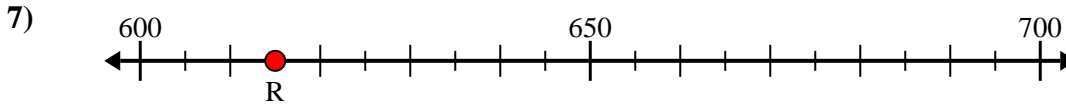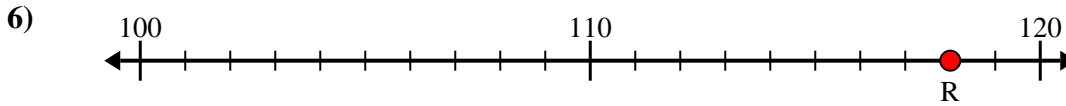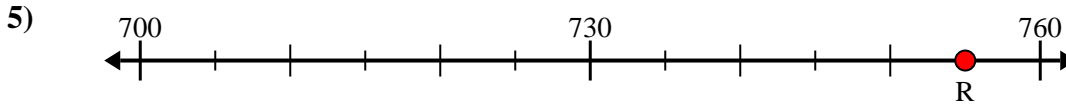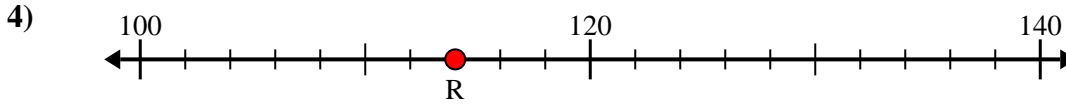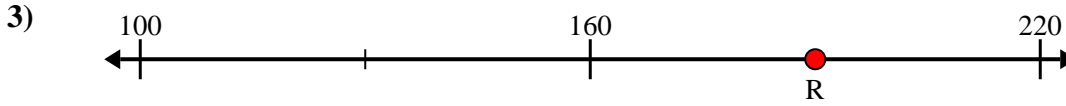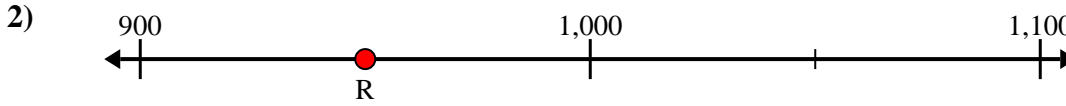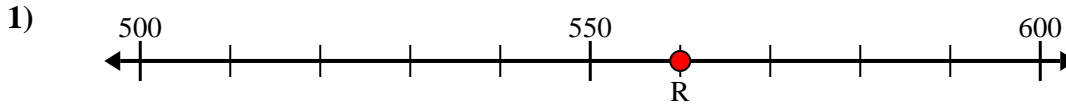

Answers

1. 560

2. 950

3. 190

4. 114

5. 755

6. 118

7. 615

8. 1,090

9. 505

10. 612