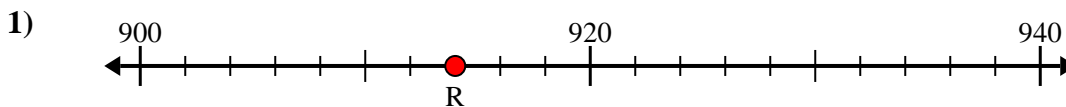





Find the value of R.


Answers




1. _____

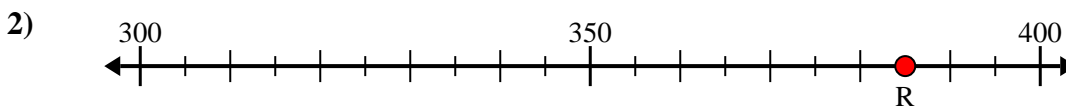


2. _____

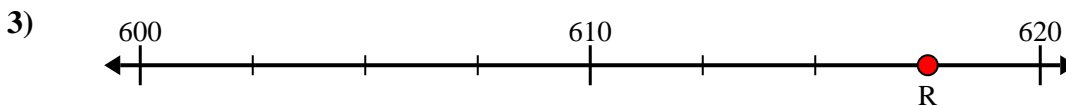


3. _____

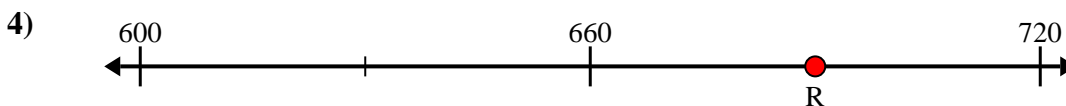


4. _____

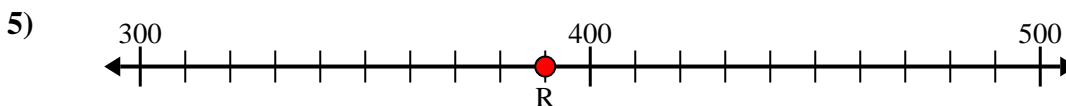


5. _____

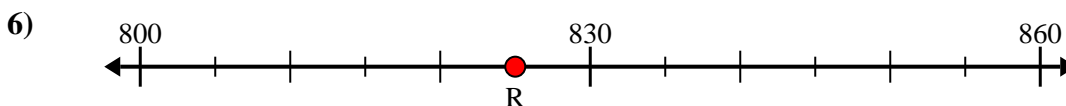


6. _____

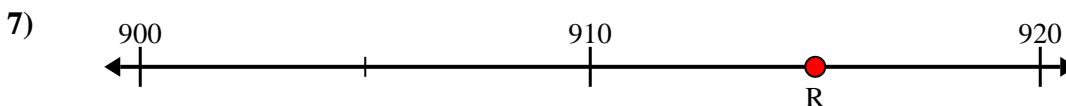


7. _____

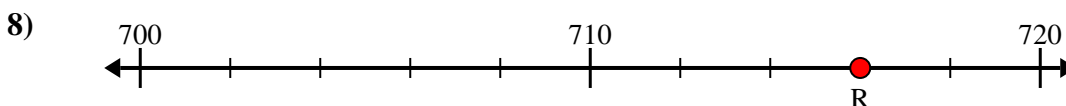

8. _____

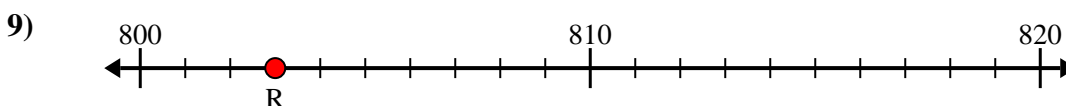











9. _____

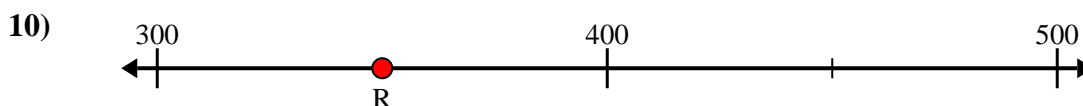

10. _____



Find the value of R.

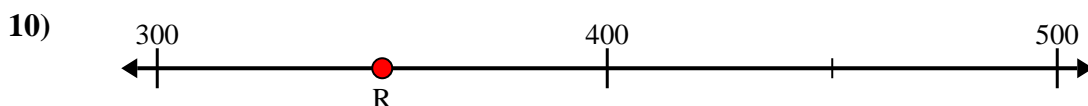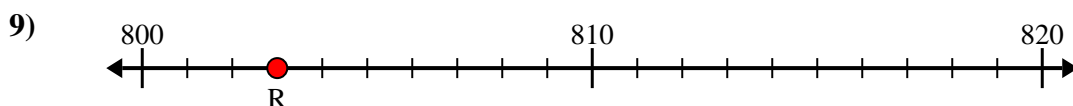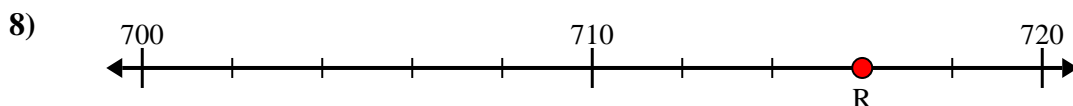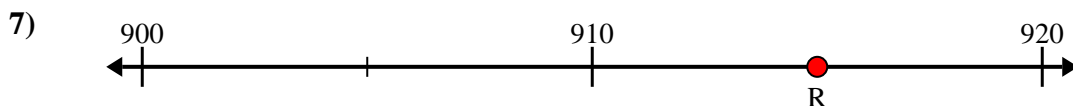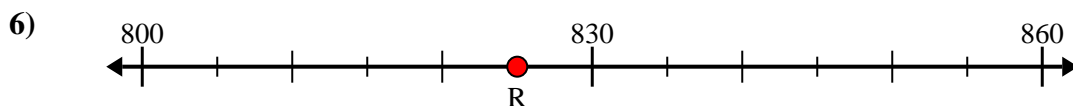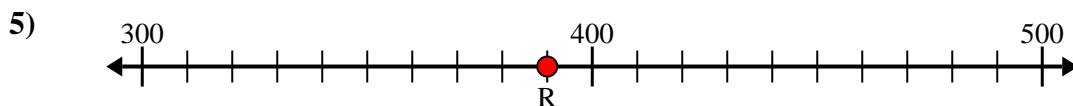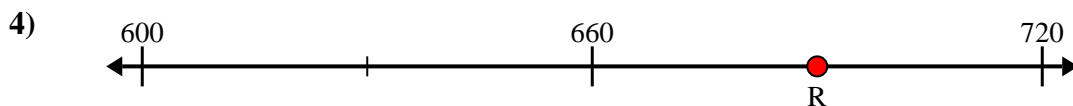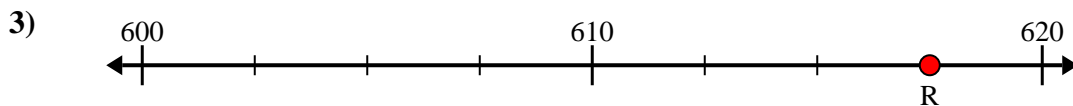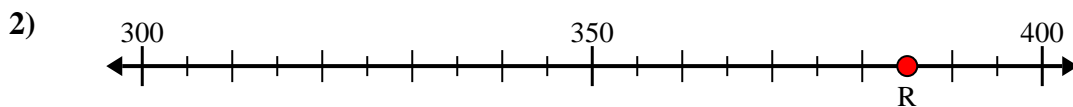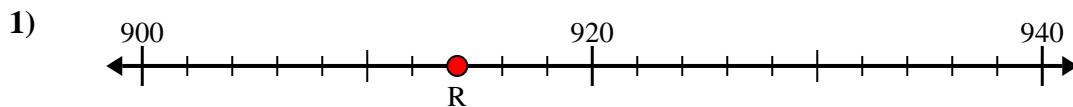

Answers

1. 914

2. 385

3. 617.5

4. 690

5. 390

6. 825

7. 915

8. 716

9. 803

10. 350