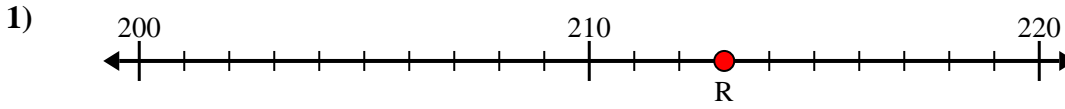





Find the value of R.


Answers




1. _____

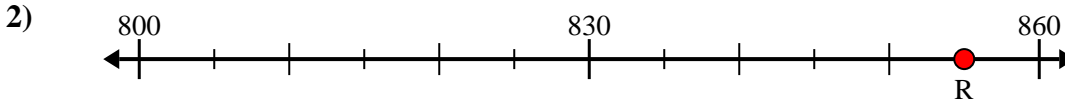


2. _____

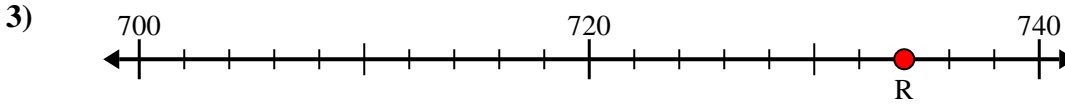


3. _____

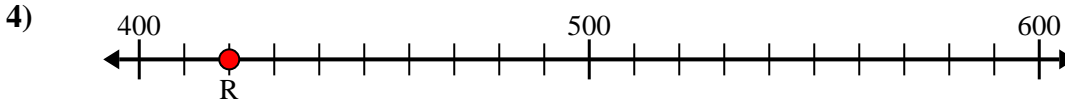


4. _____

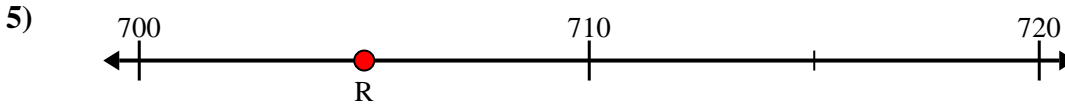


5. _____

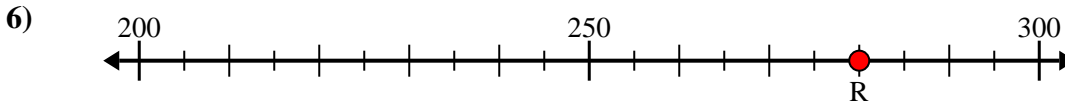


6. _____

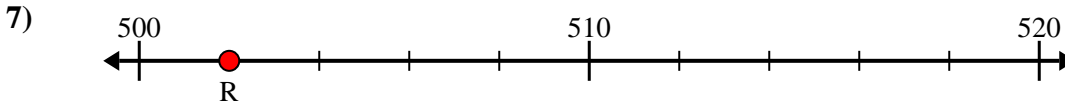


7. _____

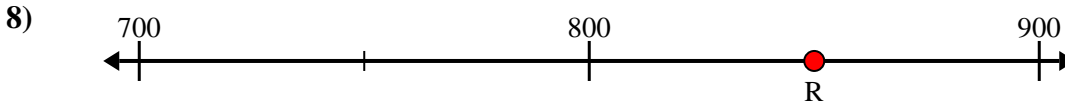

8. _____

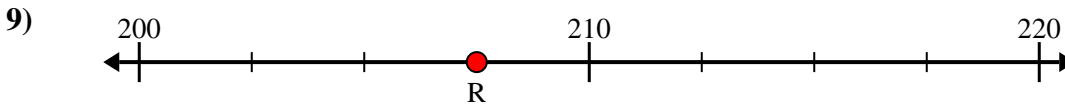











9. _____

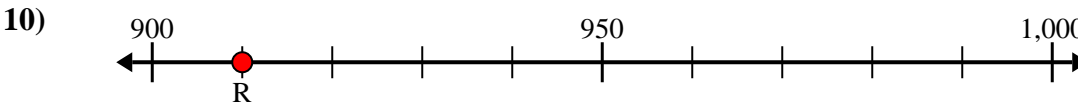

10. _____



Find the value of R.

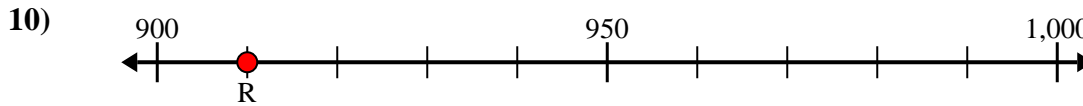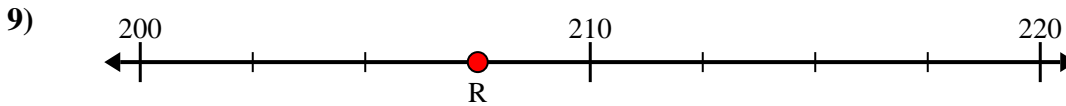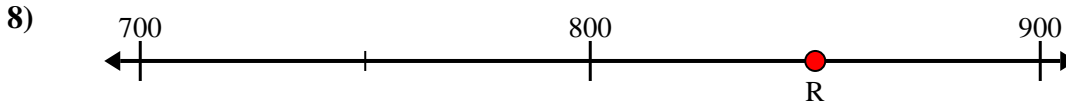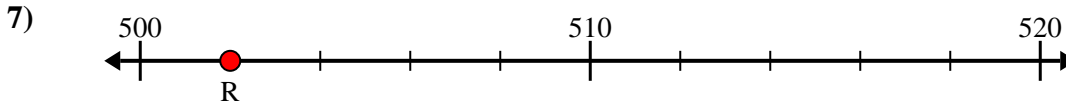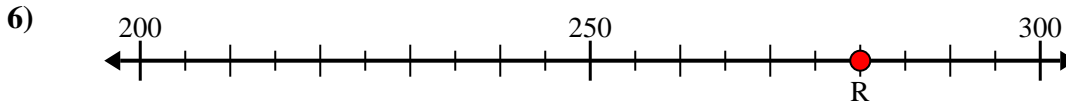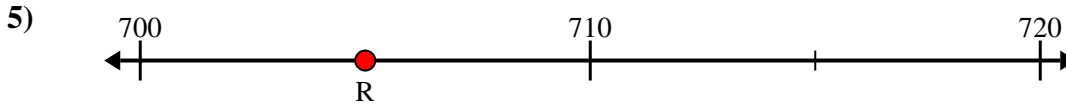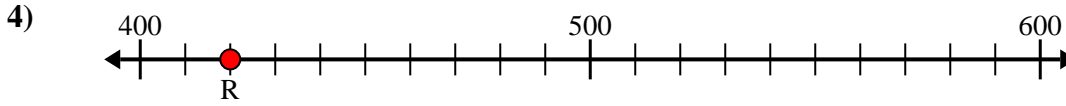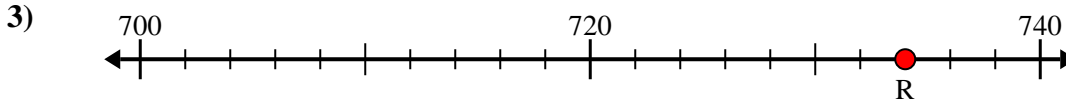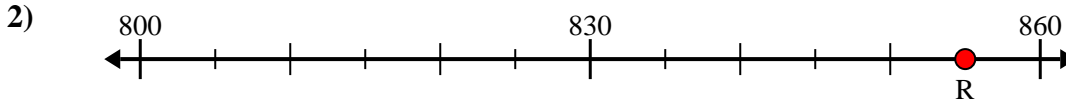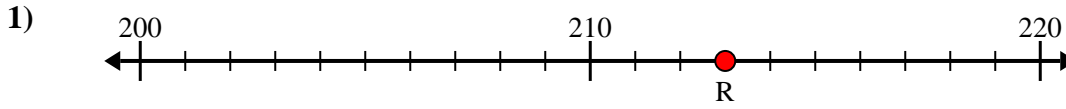

Answers

1. 213

2. 855

3. 734

4. 420

5. 705

6. 280

7. 502

8. 850

9. 207.5

10. 910