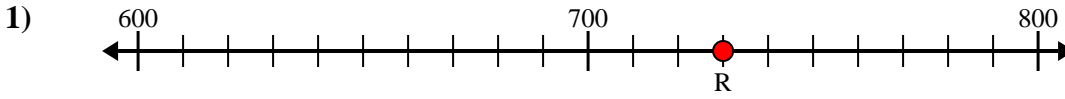





Find the value of R.


Answers




1. _____

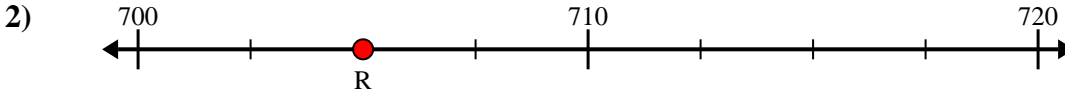


2. _____

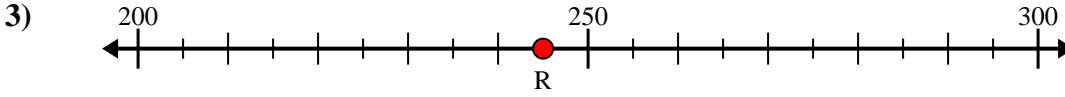


3. _____

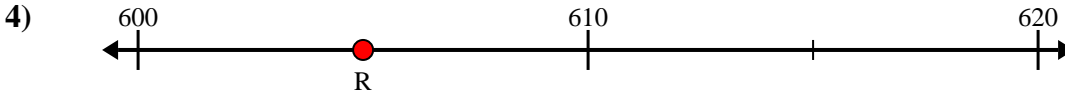


4. _____

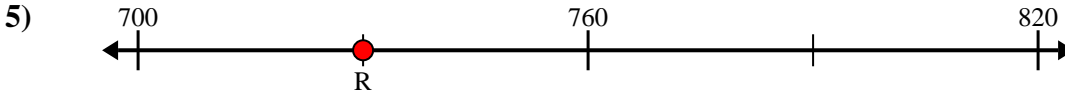


5. _____

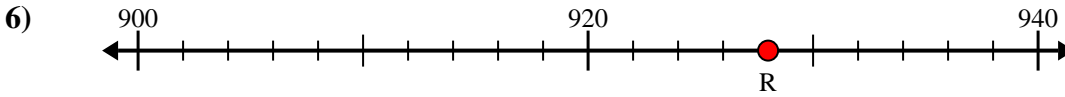


6. _____

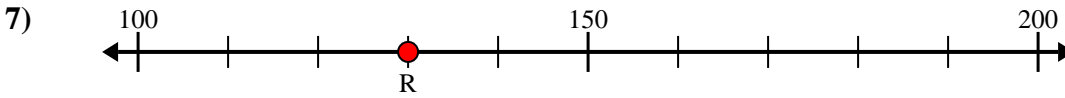


7. _____

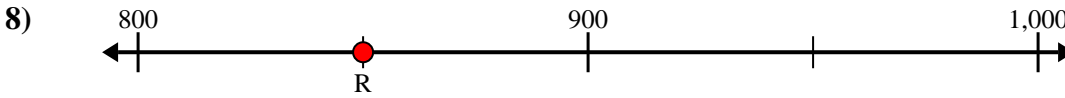

8. _____

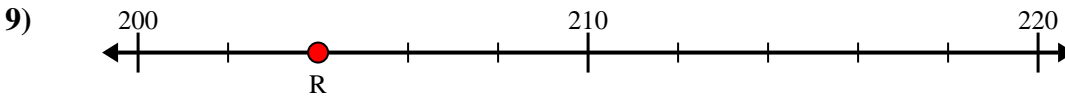











9. _____

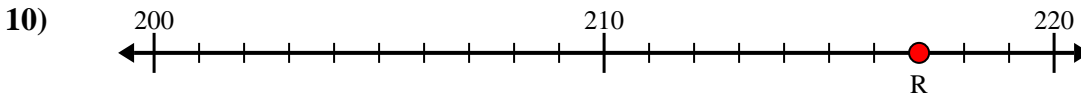

10. _____



Find the value of R.

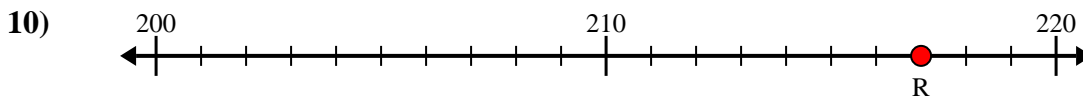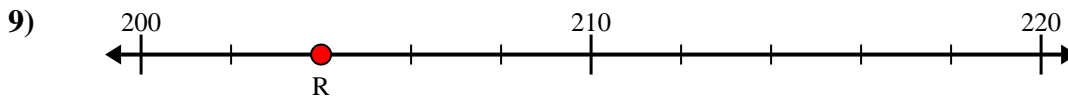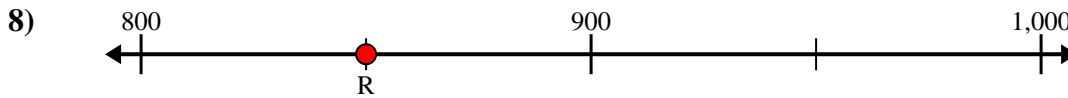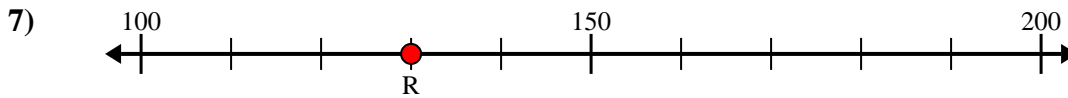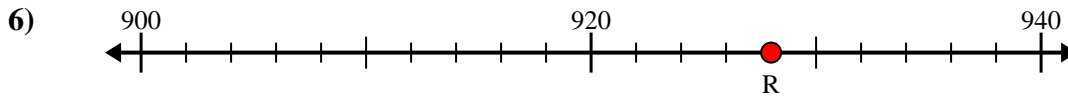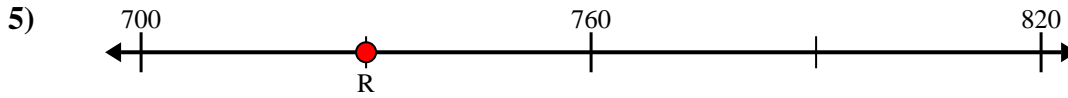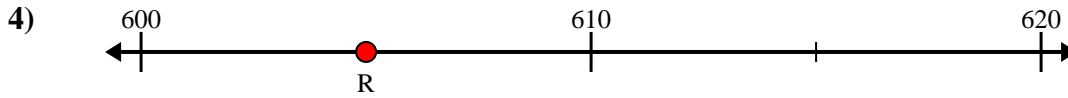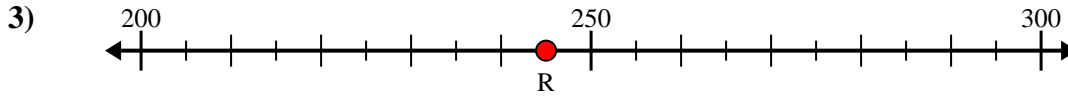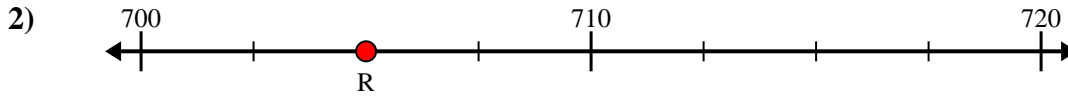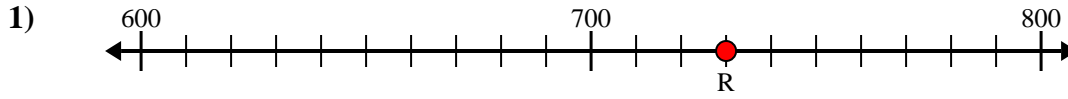

Answers

1. 730

2. 705

3. 245

4. 605

5. 730

6. 928

7. 130

8. 850


9. 204

10. 217




Find the value of R.


Answers

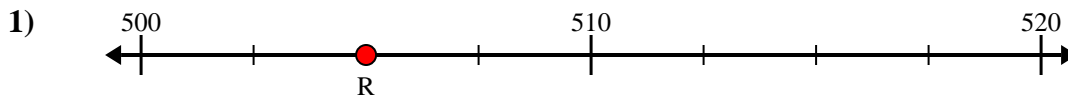


1. _____

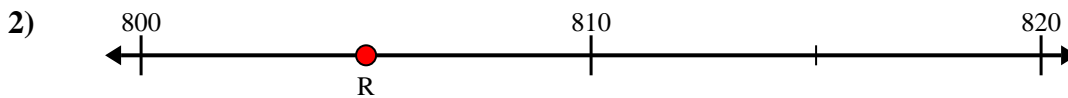


2. _____

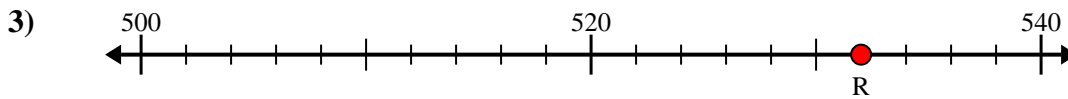


3. _____

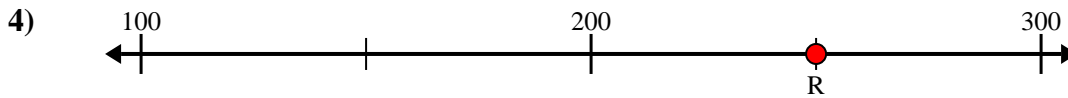


4. _____

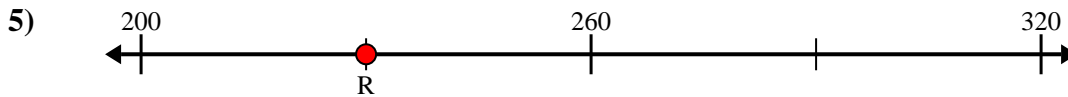


5. _____

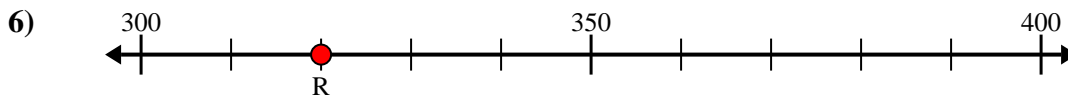


6. _____

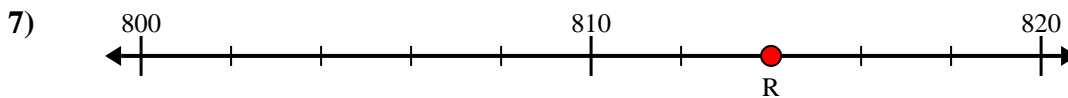


7. _____

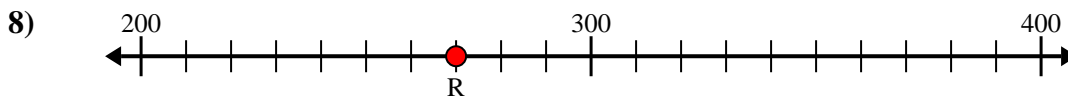

8. _____

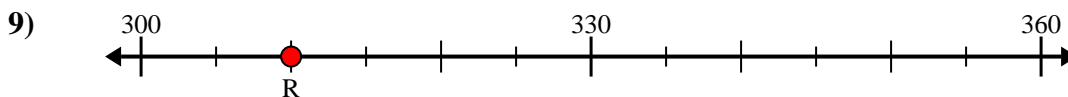











9. _____

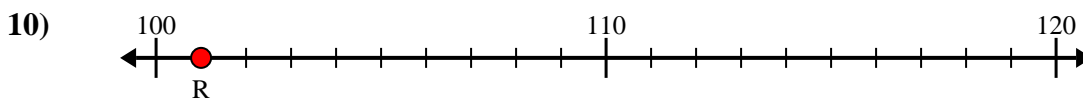

10. _____



Find the value of R.

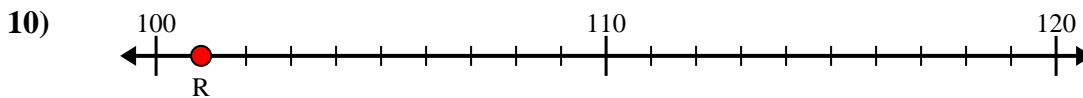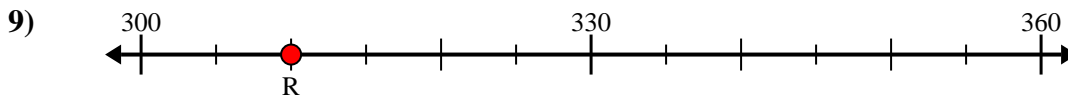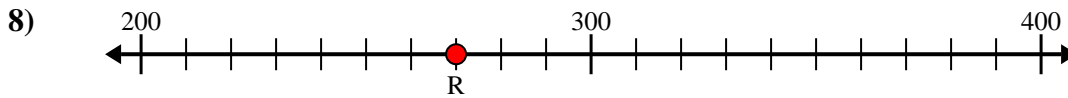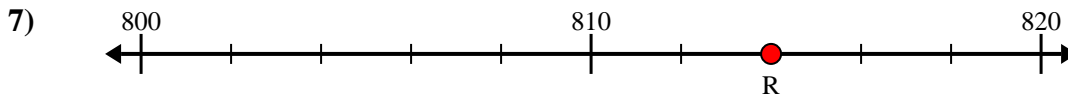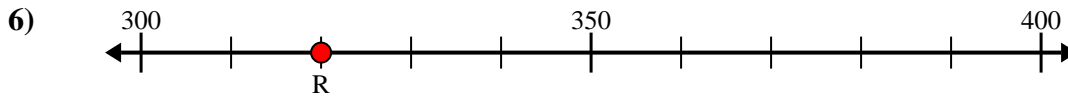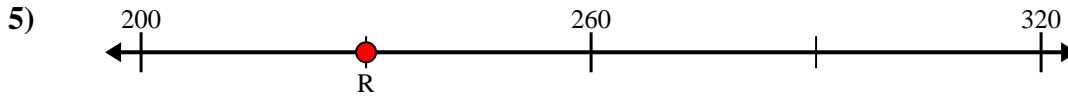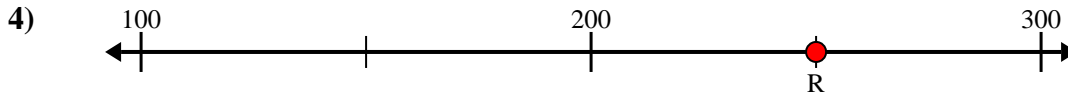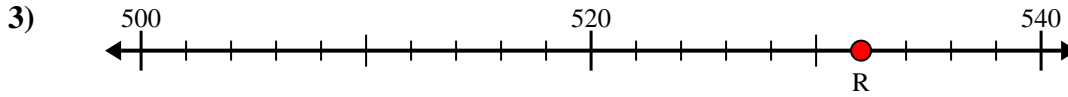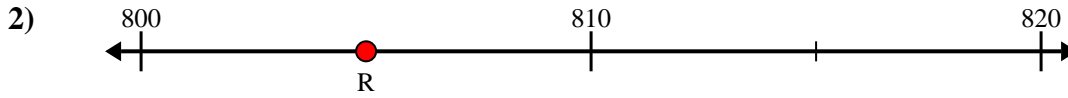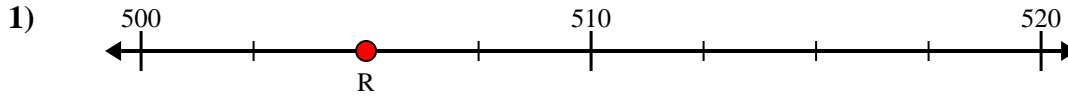

Answers

1. 505

2. 805

3. 532

4. 250

5. 230

6. 320

7. 814

8. 270


9. 310

10. 101




Find the value of R.


Answers

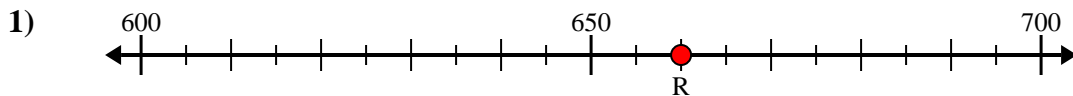


1. _____

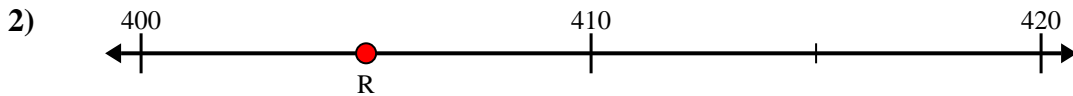


2. _____

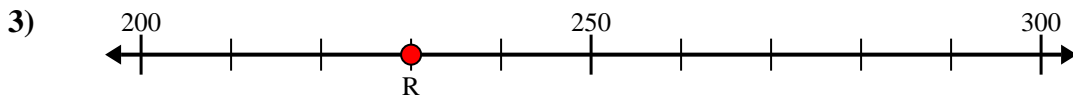


3. _____

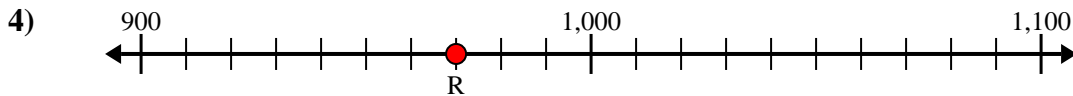


4. _____

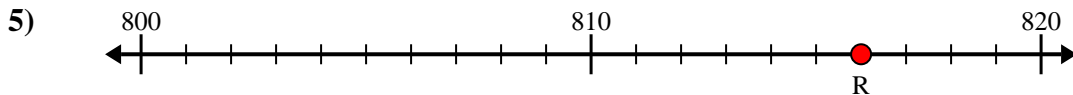

5. _____

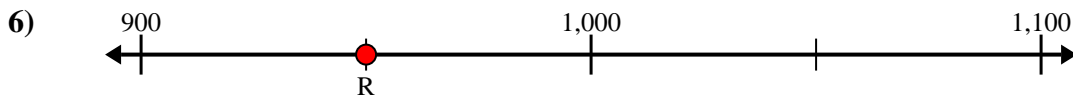


6. _____

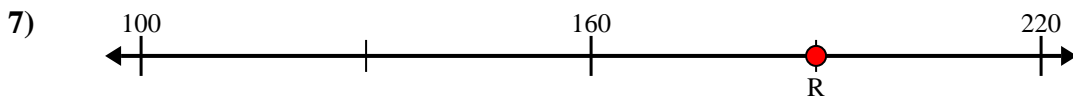


7. _____



8. _____

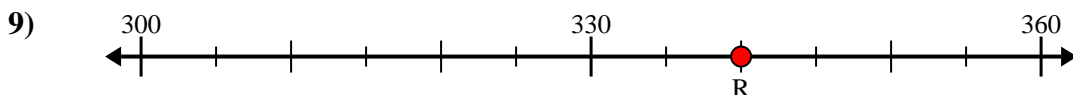


9. _____

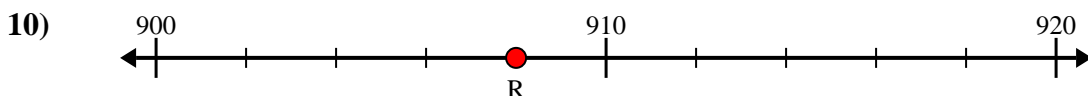

10. _____



Find the value of R.

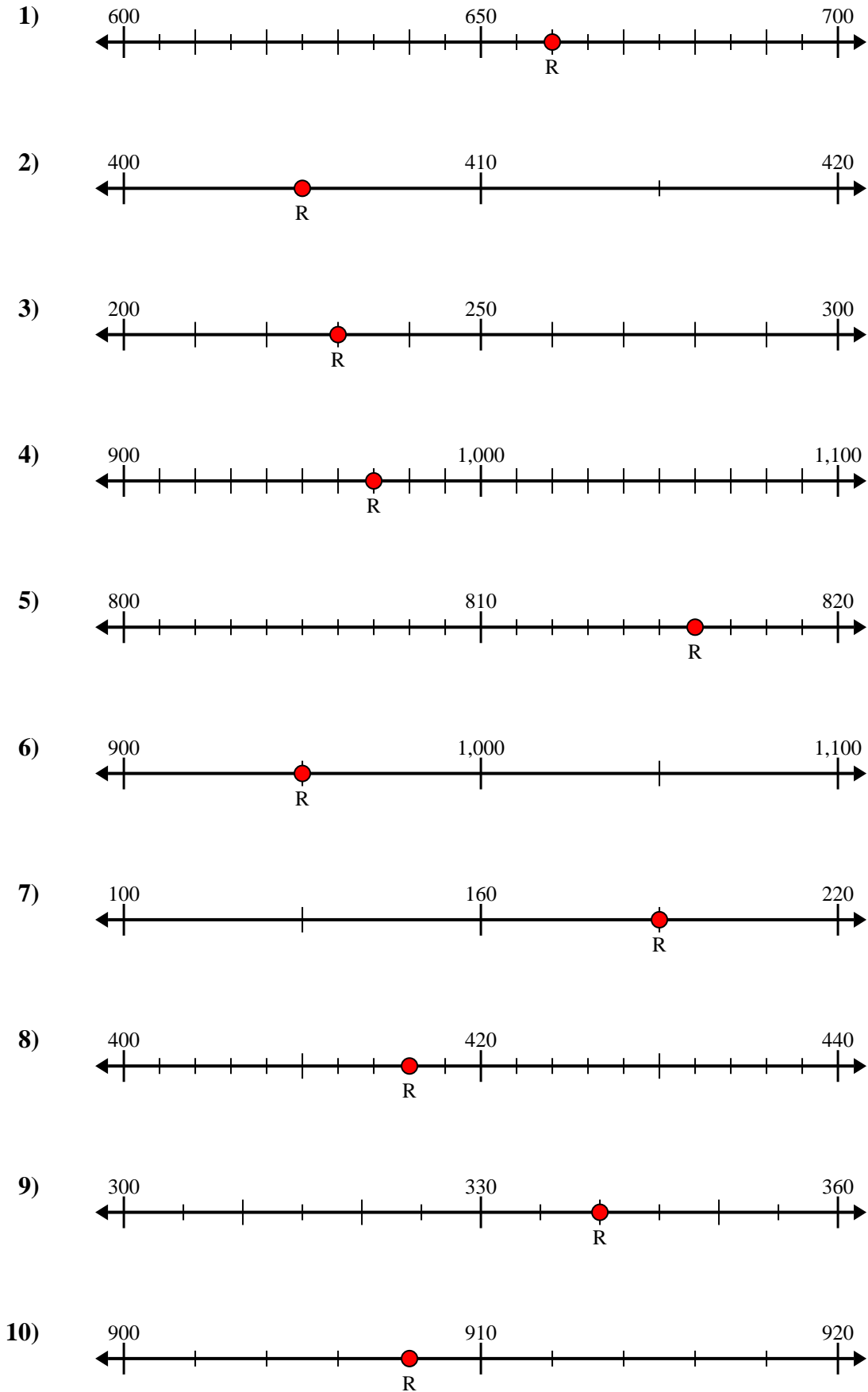


Answers

1. 660
2. 405
3. 230
4. 970
5. 816
6. 950
7. 190
8. 416
9. 340
10. 908




Find the value of R.


Answers

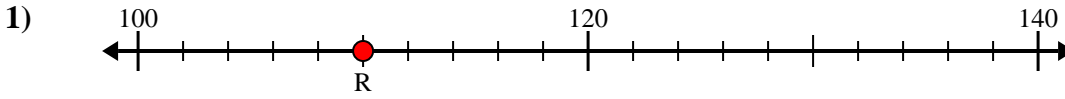


1. _____

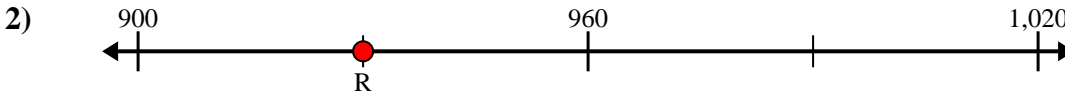


2. _____

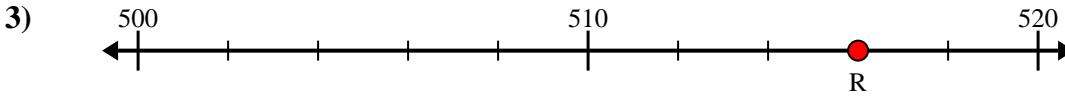


3. _____

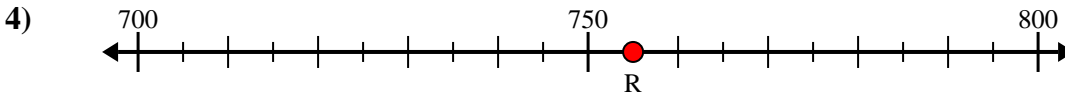


4. _____

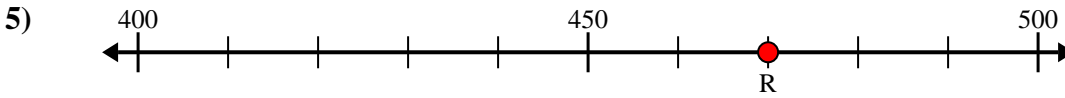


5. _____

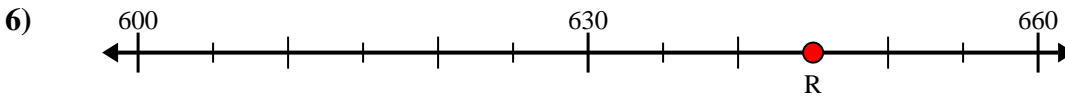


6. _____

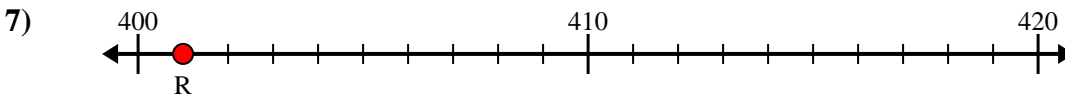


7. _____

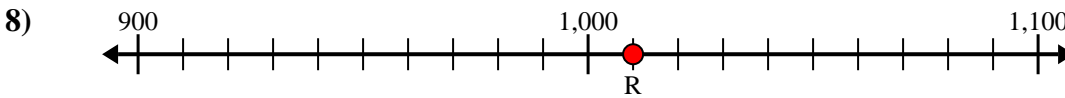

8. _____

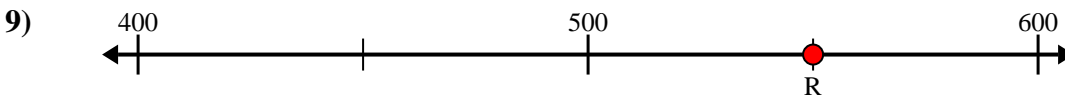


9. _____

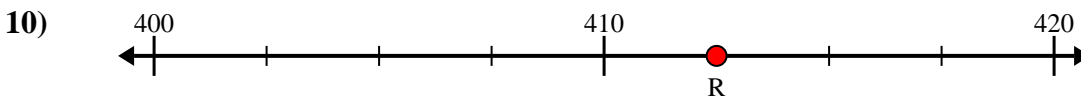

10. _____



Find the value of R.

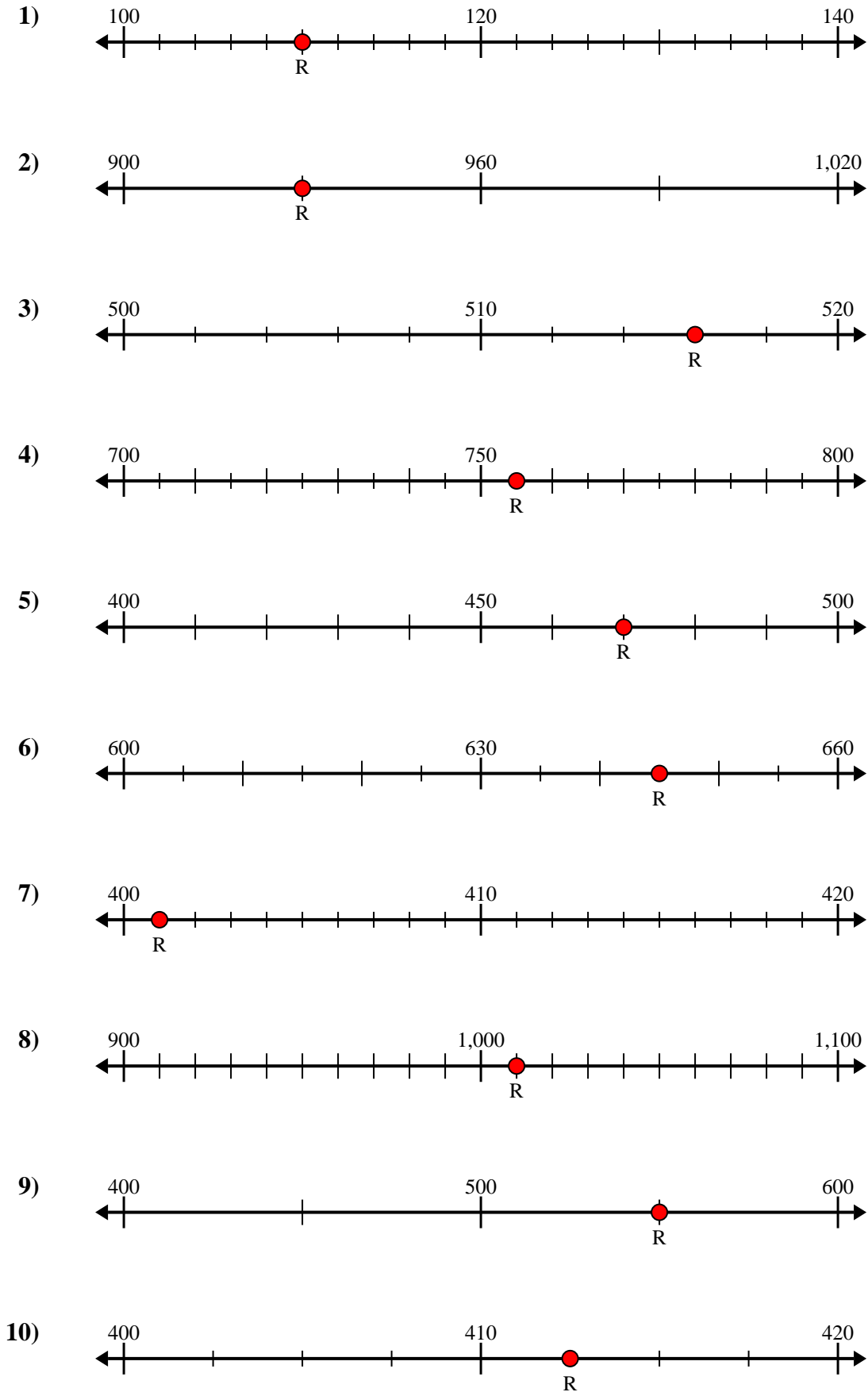


Answers

1. 110
2. 930
3. 516
4. 755
5. 470
6. 645
7. 401
8. 1,010
9. 550
10. 413




Find the value of R.


Answers

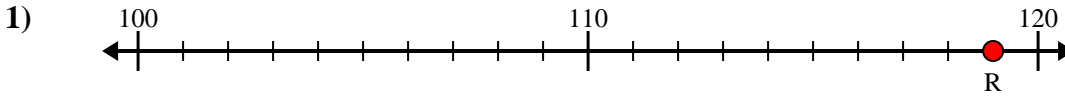


1. _____

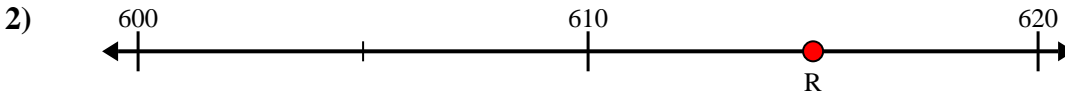


2. _____

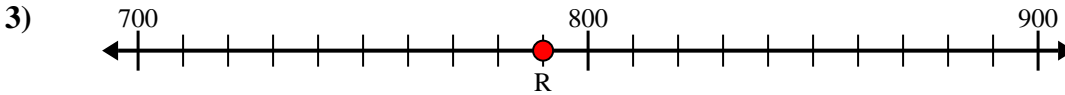


3. _____

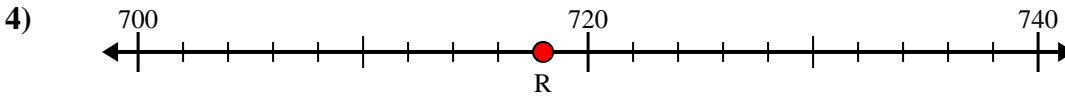


4. _____

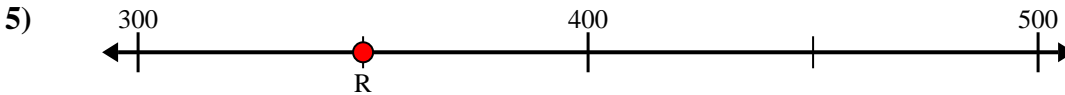


5. _____

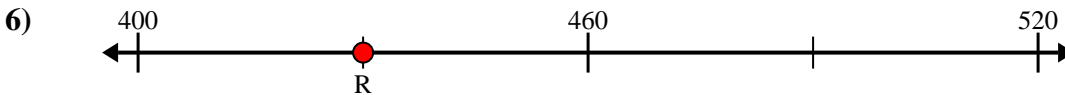


6. _____

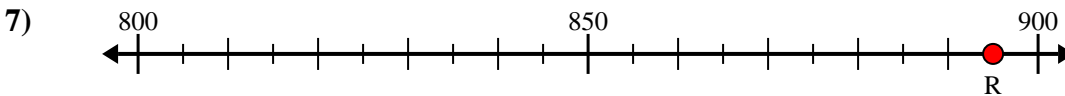


7. _____

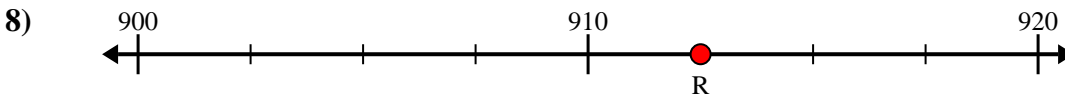

8. _____

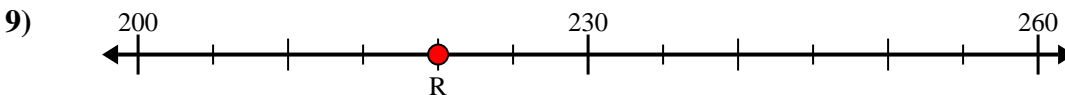











9. _____

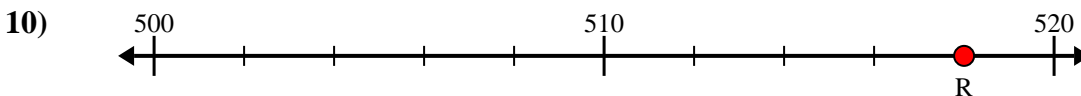

10. _____



Find the value of R.

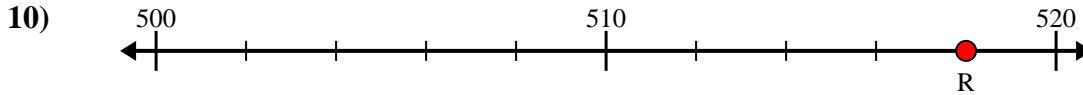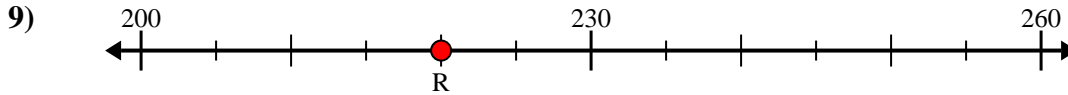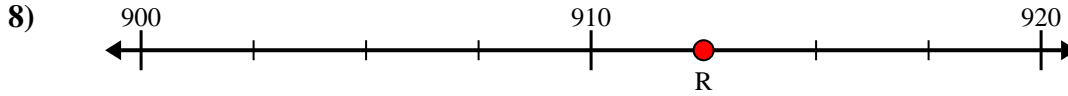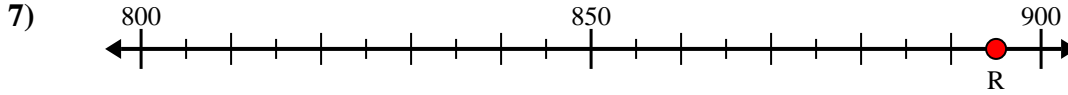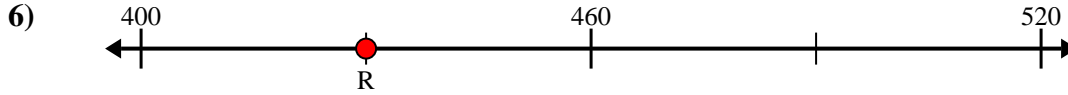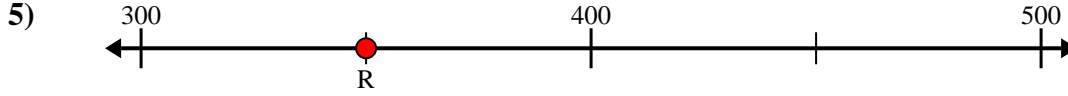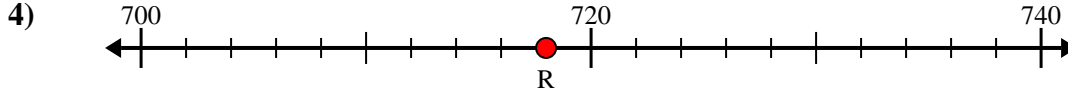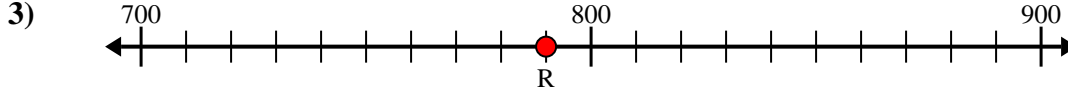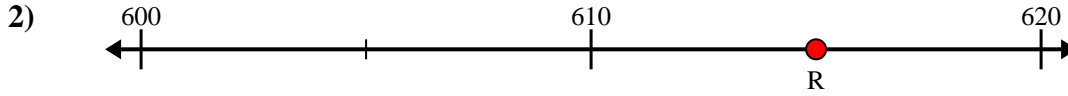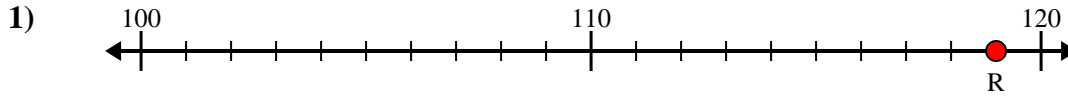

Answers

1. 119

2. 615

3. 790

4. 718

5. 350

6. 430

7. 895

8. 913


9. 220

10. 518




Find the value of R.


Answers

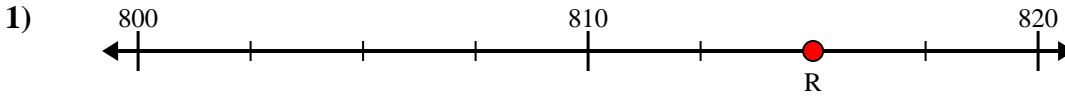


1. _____

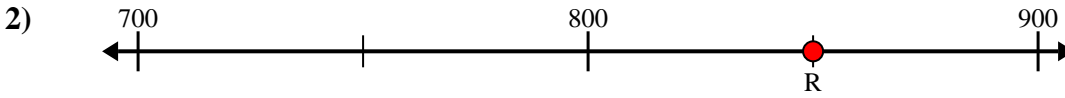


2. _____

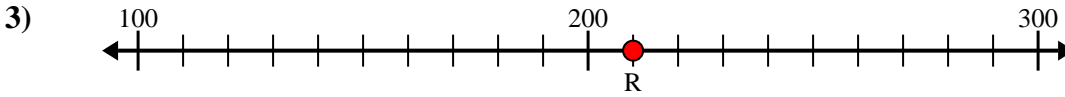


3. _____

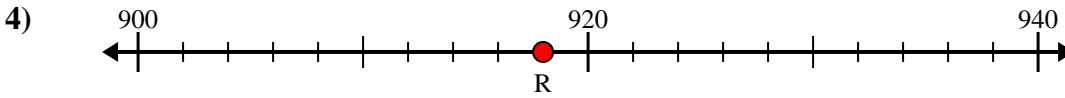


4. _____

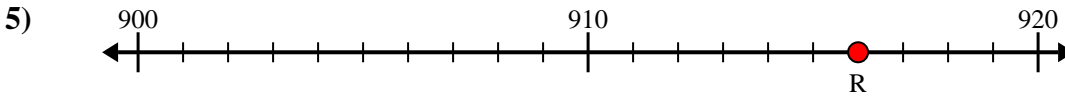


5. _____

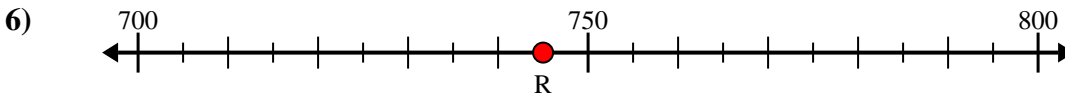


6. _____

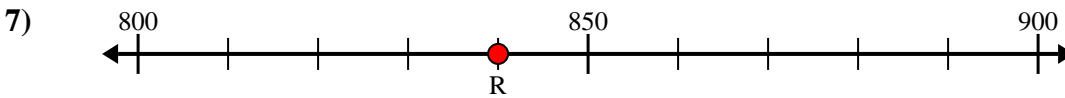


7. _____

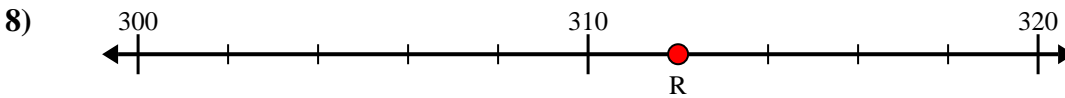

8. _____

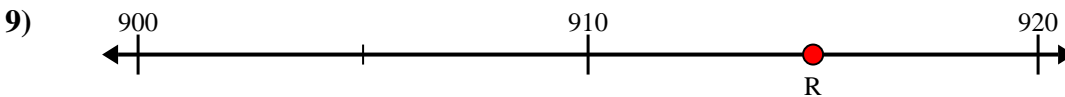


9. _____

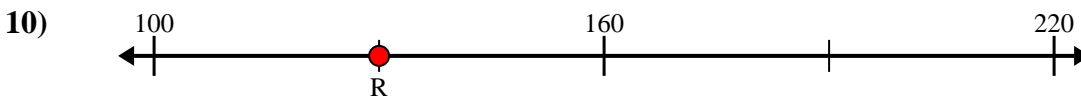

10. _____



Find the value of R.

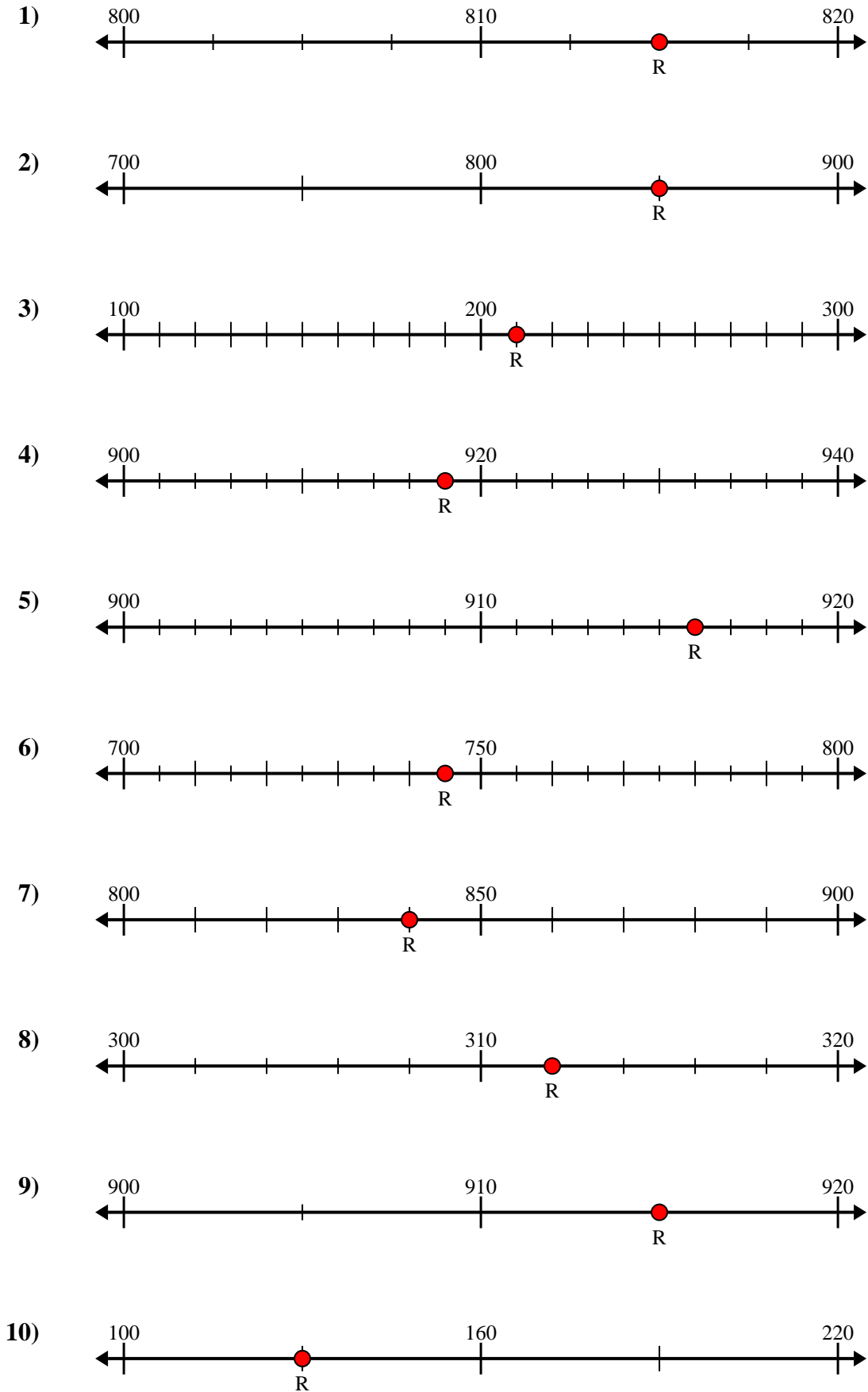


Answers

1. 815
2. 850
3. 210
4. 918
5. 916
6. 745
7. 840
8. 312
9. 915
10. 130




Find the value of R.


Answers

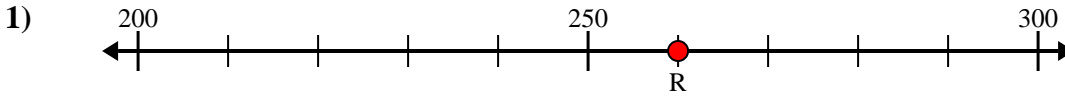


1. _____

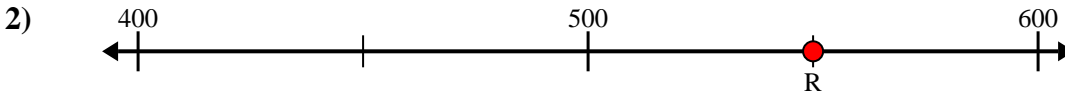


2. _____

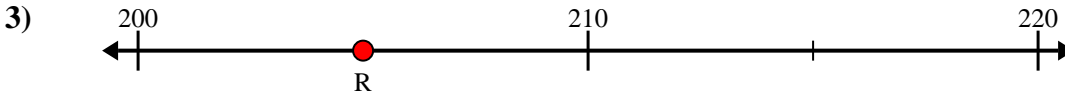


3. _____

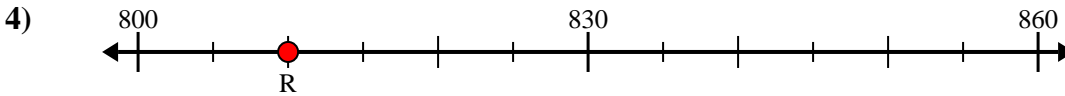


4. _____

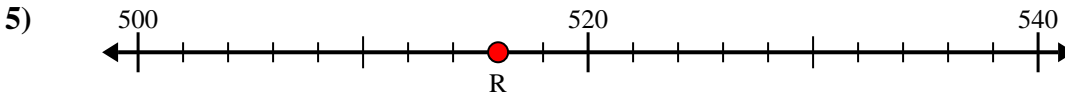


5. _____

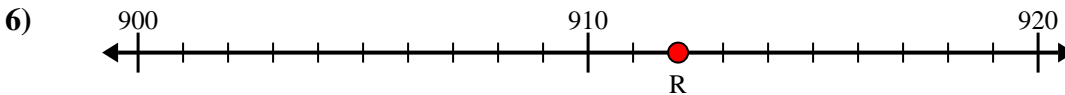


6. _____

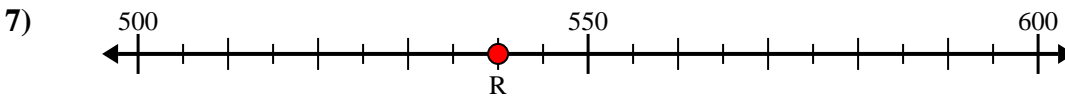


7. _____

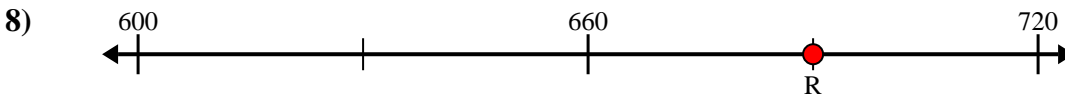

8. _____

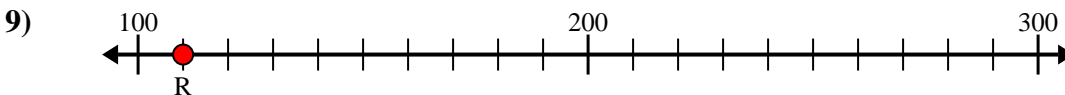










9. _____

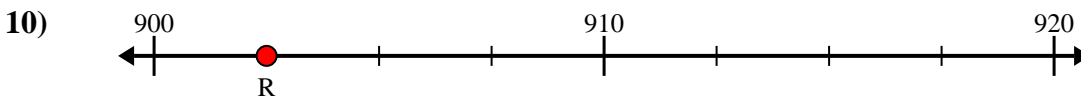

10. _____



Find the value of R.

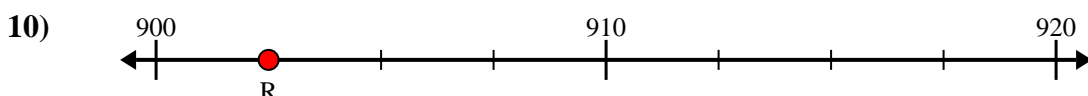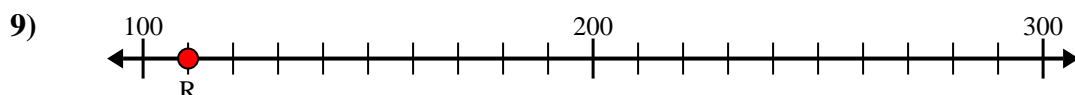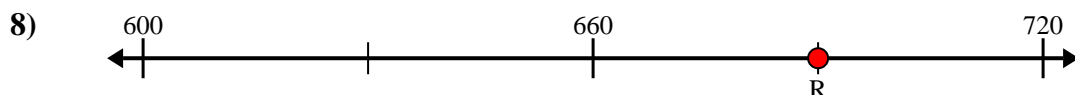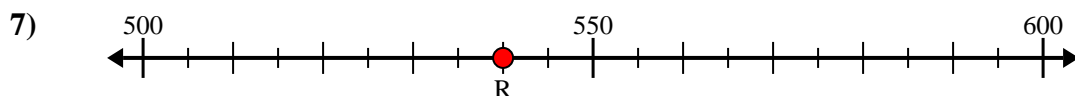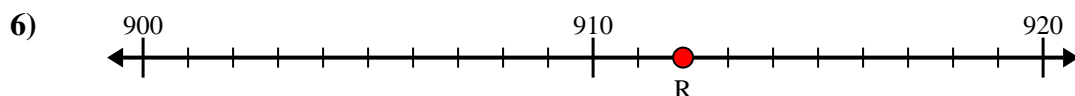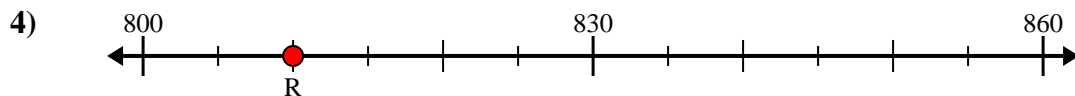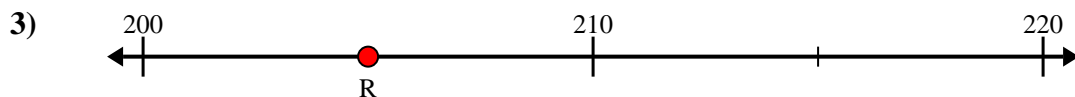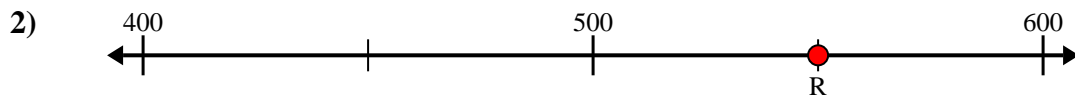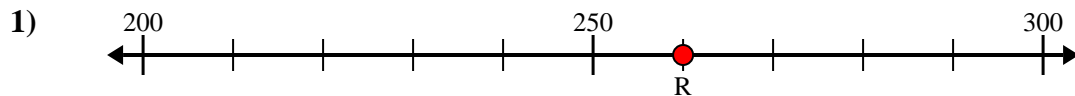

Answers

1. 260

2. 550

3. 205

4. 810

5. 516

6. 912

7. 540











8. 690

9. 110

10. 903



Find the value of R.

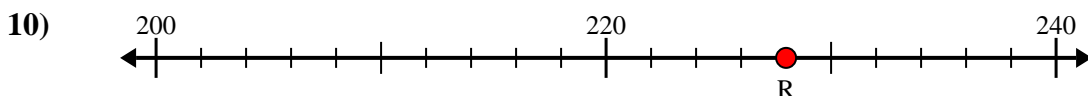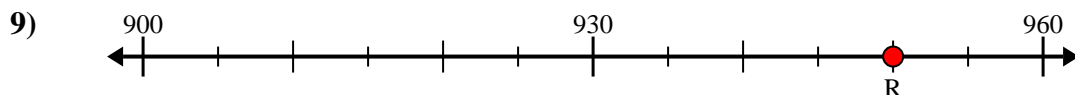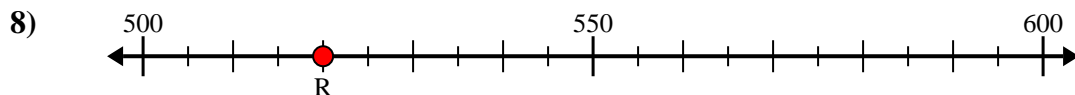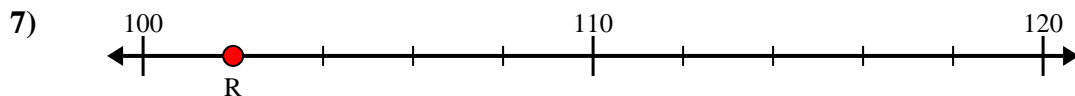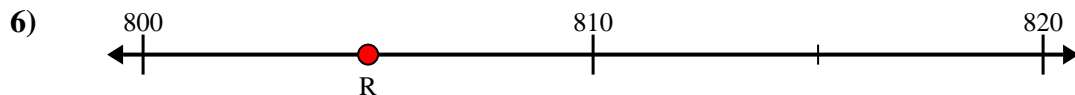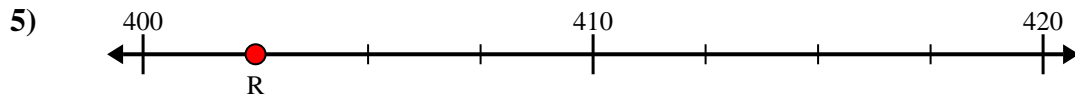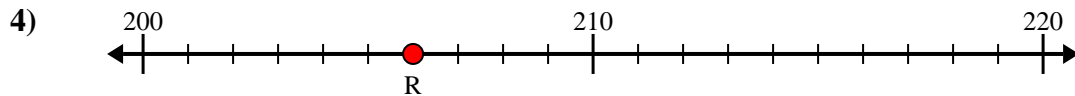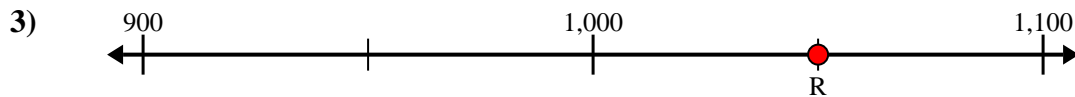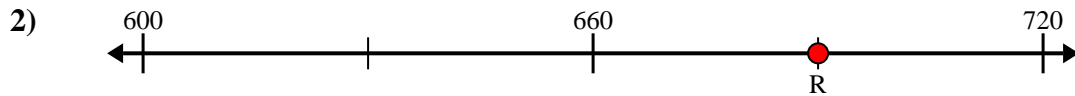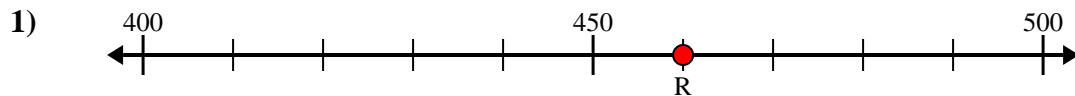

Answers

1. _____

2. _____

3. _____

4. _____

5. _____

6. _____

7. _____











8. _____

9. _____

10. _____



Find the value of R.

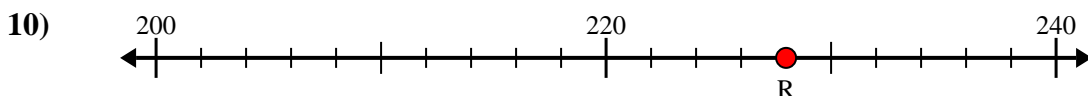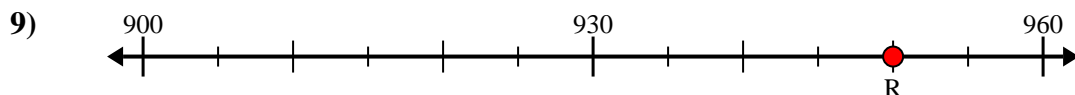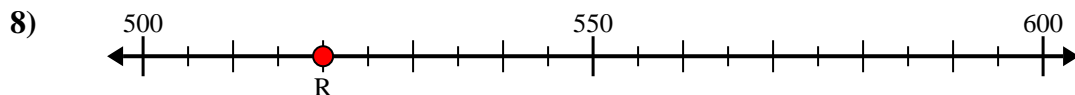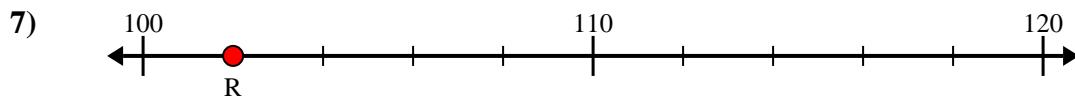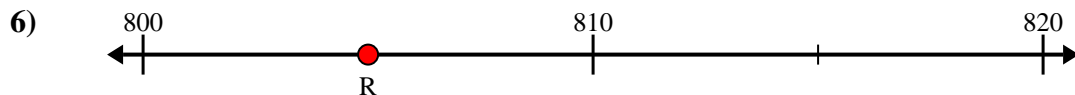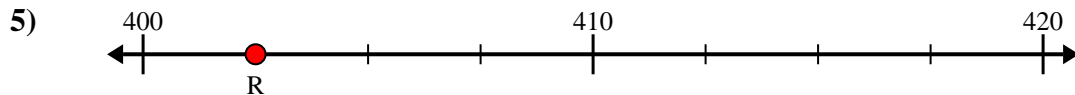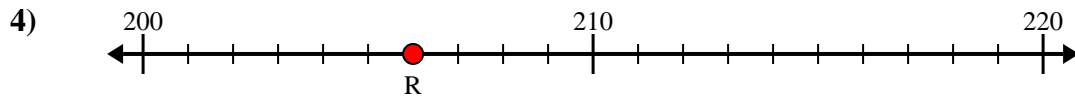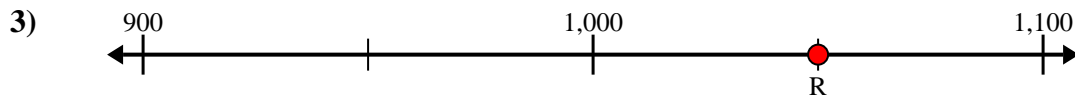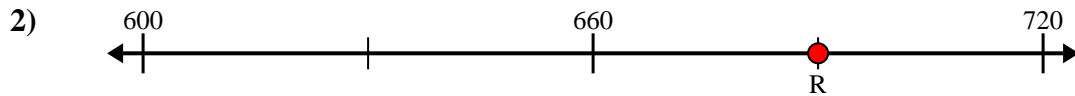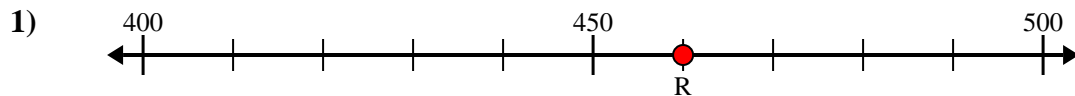

Answers

1. 460

2. 690

3. 1,050

4. 206

5. 403

6. 805

7. 102

8. 520


9. 950

10. 228




Find the value of R.


Answers

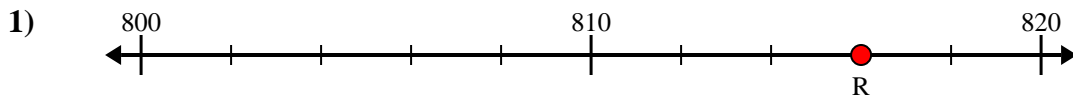


1. _____

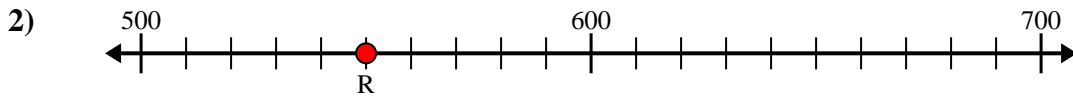


2. _____

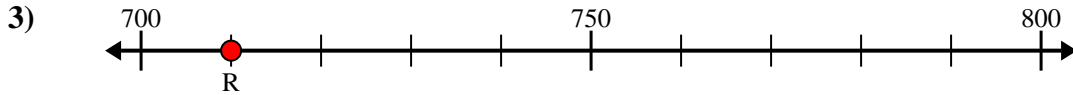


3. _____

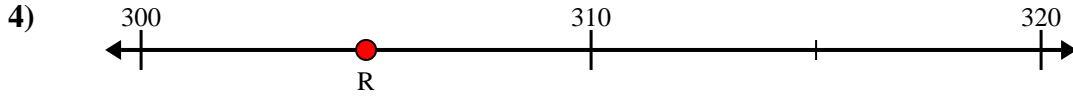


4. _____

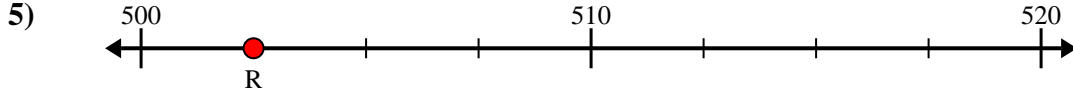


5. _____

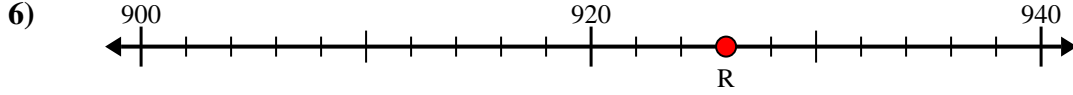


6. _____

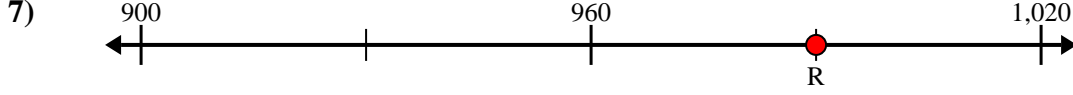


7. _____

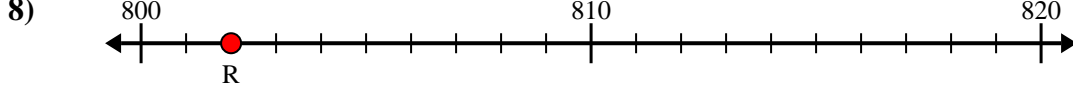

8. _____

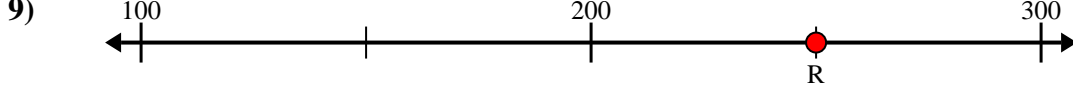











9. _____

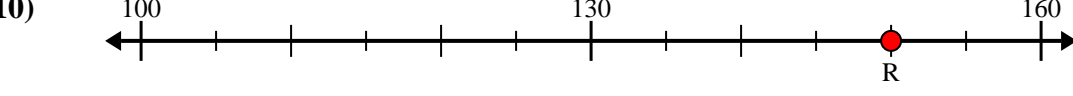

10. _____



Find the value of R.

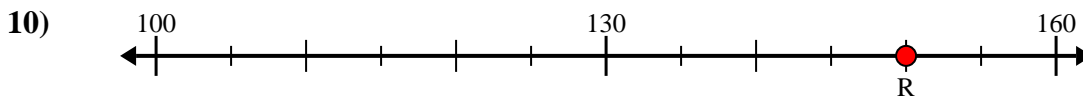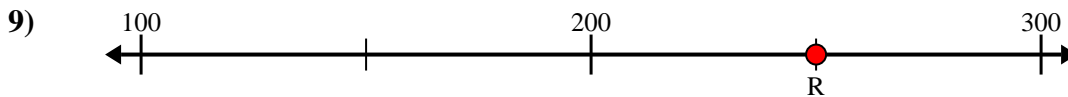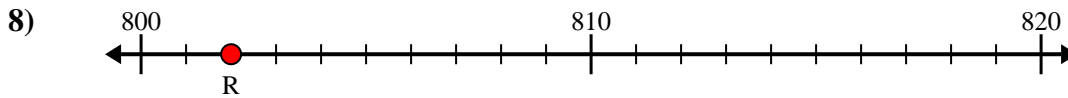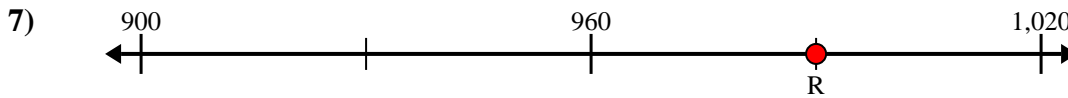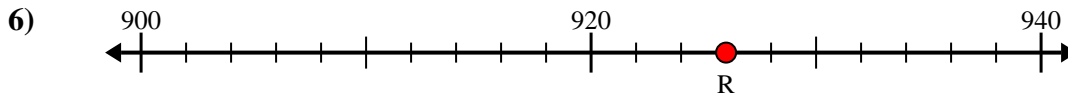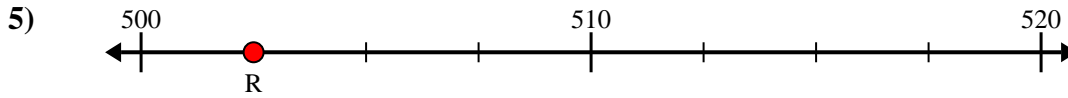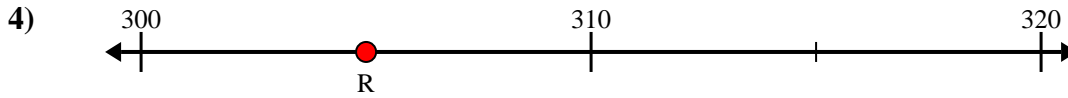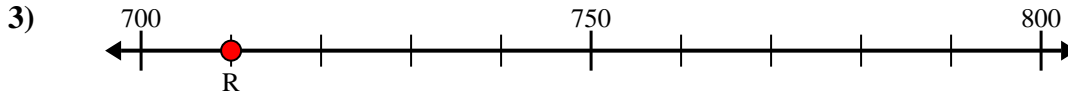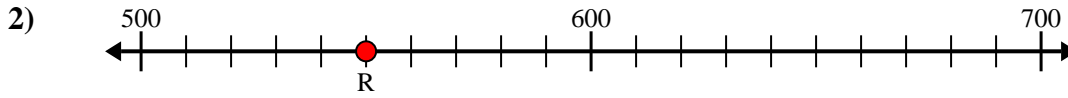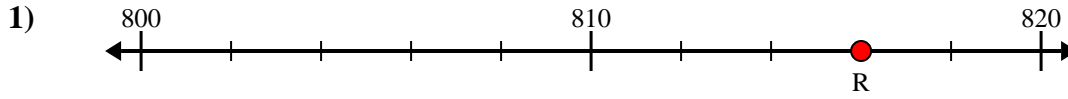

Answers

1. 816

2. 550

3. 710

4. 305

5. 503

6. 926

7. 990

8. 802


9. 250

10. 150




Find the value of R.


Answers

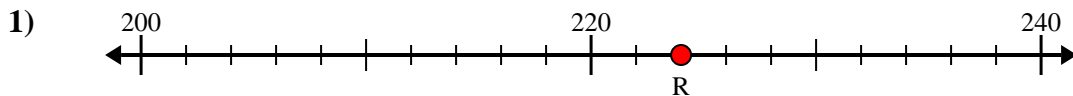


1. _____

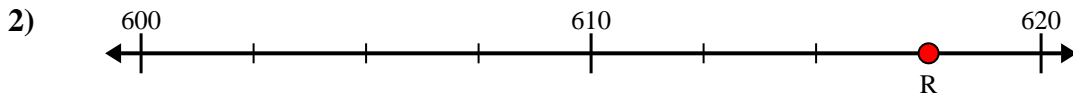


2. _____

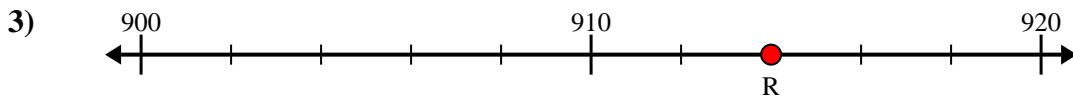


3. _____

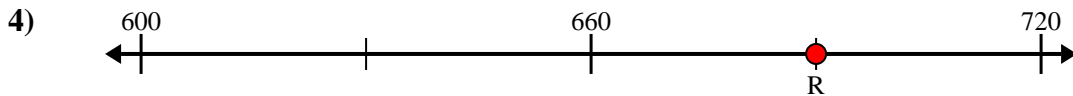


4. _____

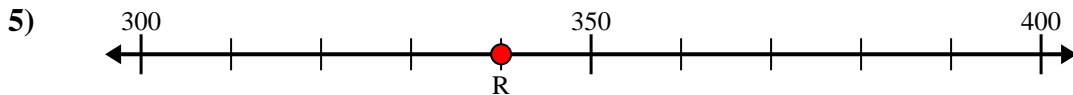


5. _____

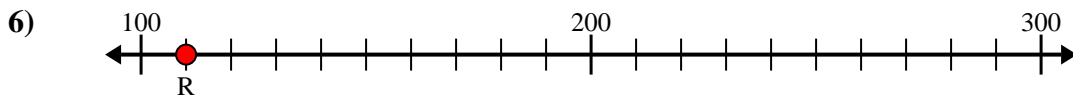


6. _____

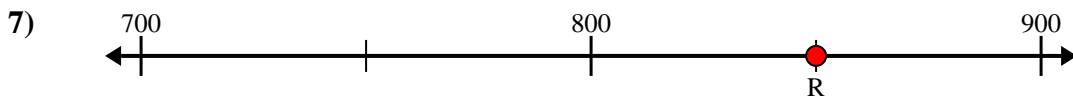


7. _____

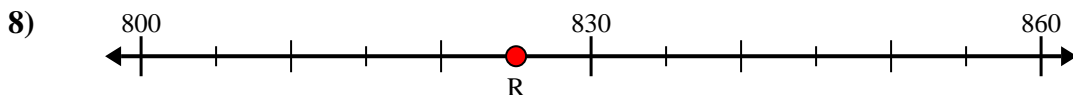

8. _____

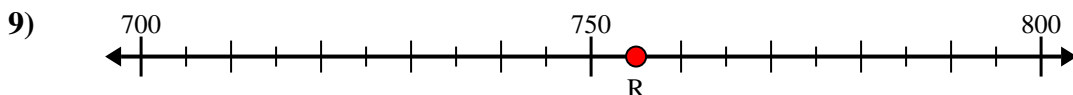


9. _____

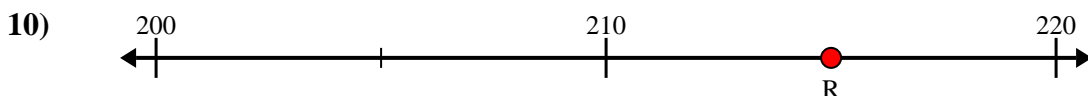

10. _____



Find the value of R.

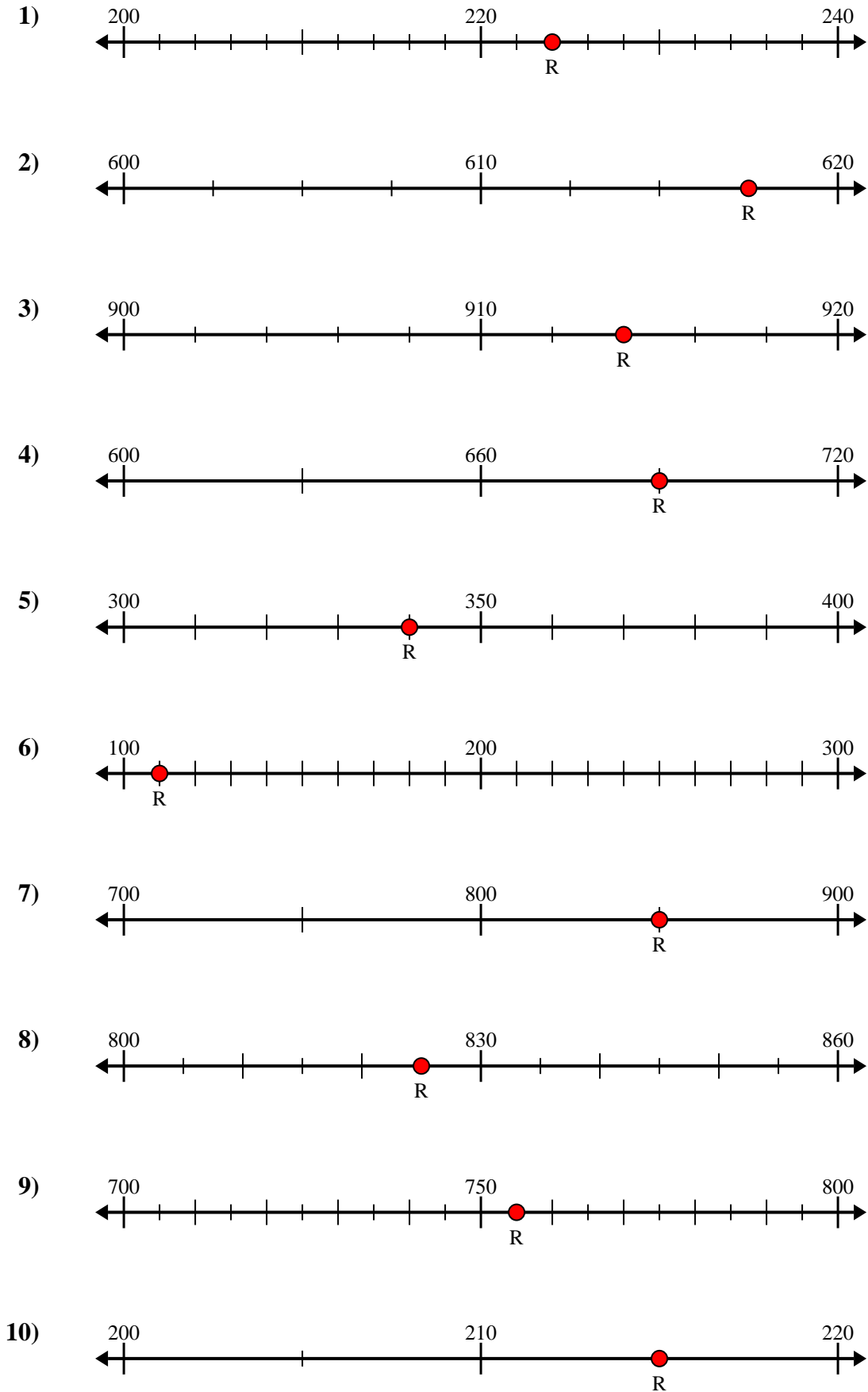

Answers

1. 224
2. 618
3. 914
4. 690
5. 340
6. 110
7. 850
8. 825
9. 755
10. 215