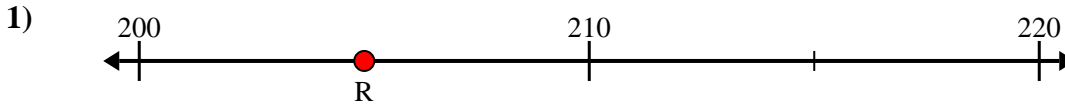





Find the value of R.


Answers




1. \_\_\_\_\_

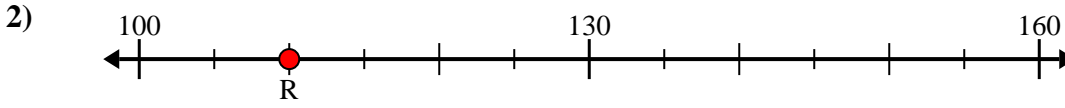


2. \_\_\_\_\_

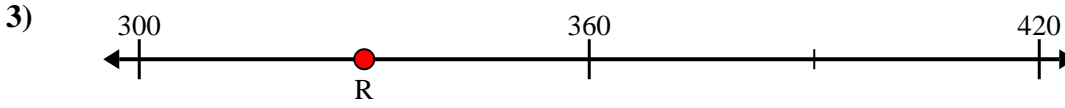


3. \_\_\_\_\_

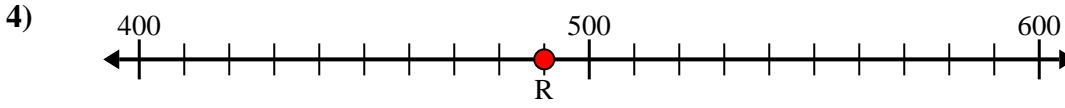


4. \_\_\_\_\_

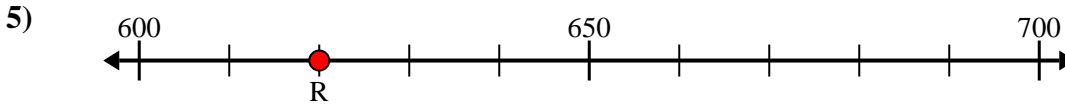


5. \_\_\_\_\_

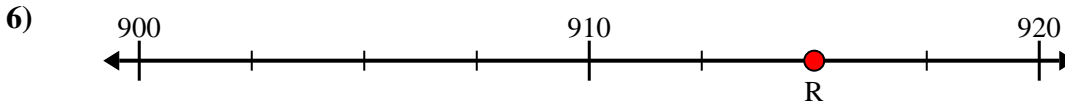


6. \_\_\_\_\_

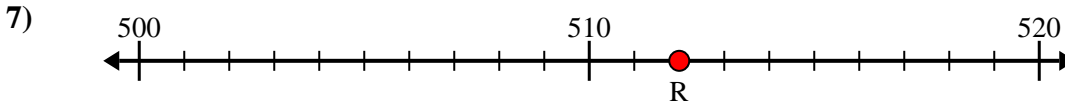


7. \_\_\_\_\_

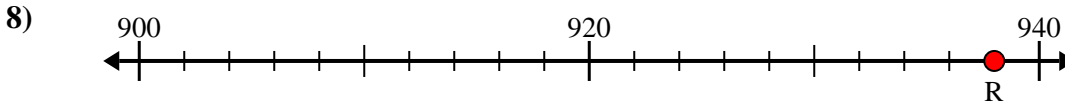

8. \_\_\_\_\_

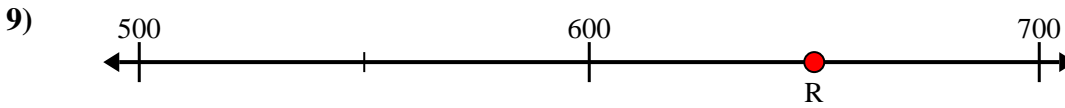











9. \_\_\_\_\_

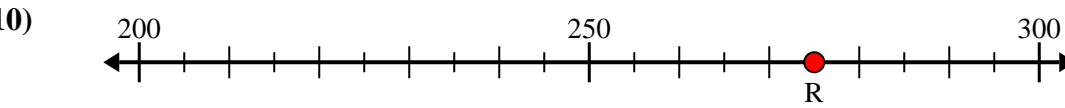

10. \_\_\_\_\_



Find the value of R.

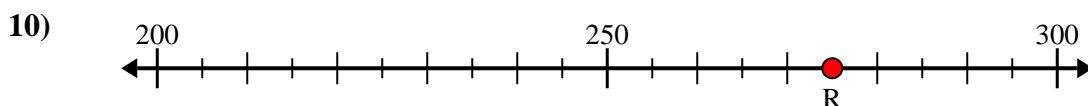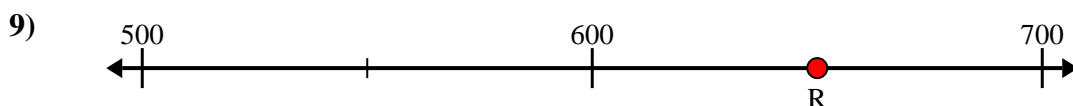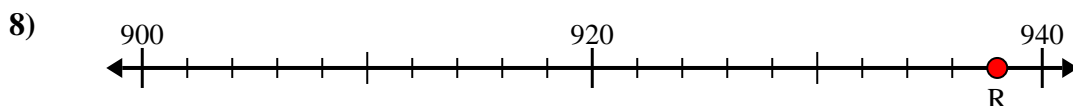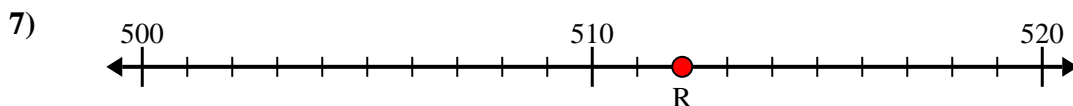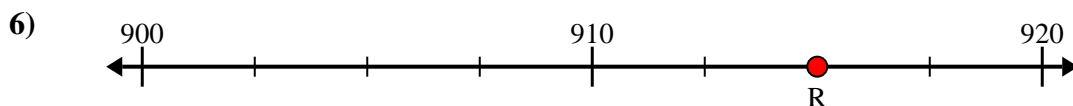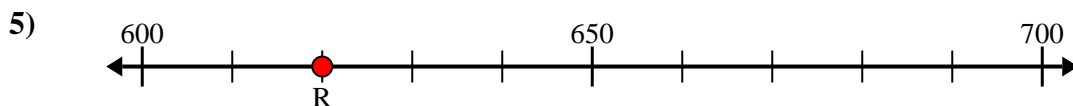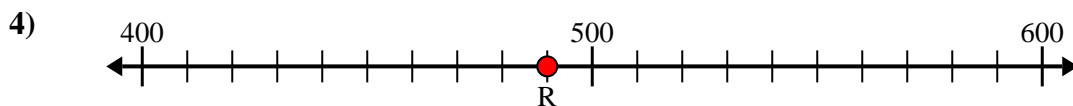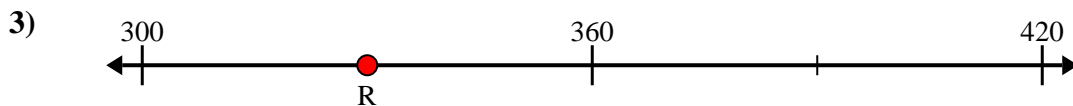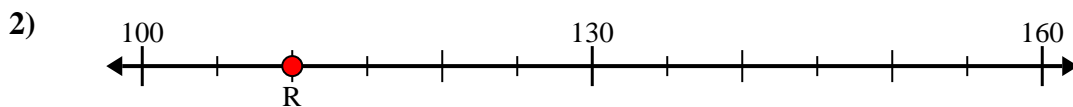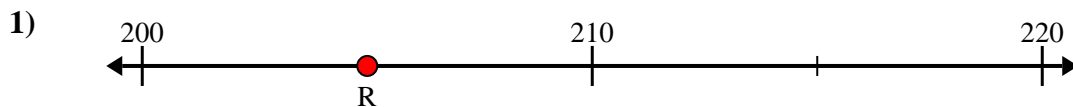

Answers

1. 205

2. 110

3. 330

4. 490

5. 620

6. 915

7. 512

8. 938


9. 650

10. 275



Find the value of R.


Answers

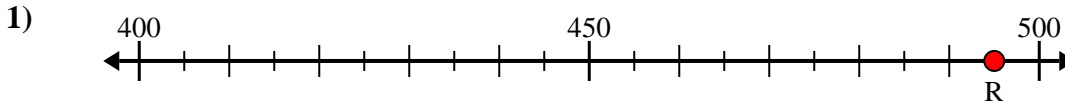


1. \_\_\_\_\_




2. \_\_\_\_\_

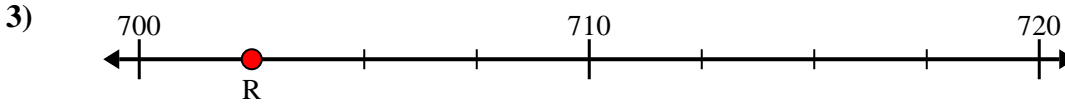


3. \_\_\_\_\_

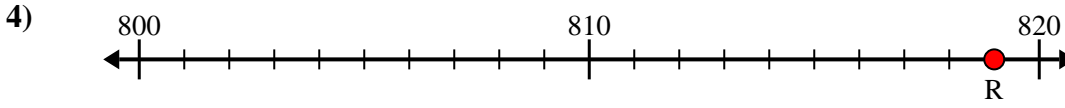

4. \_\_\_\_\_

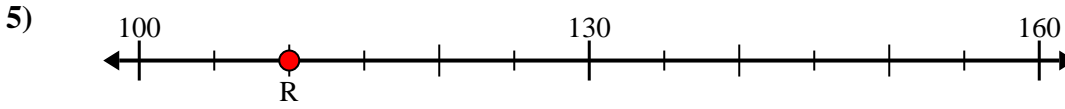


5. \_\_\_\_\_

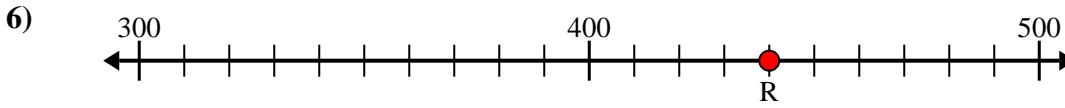


6. \_\_\_\_\_




7. \_\_\_\_\_

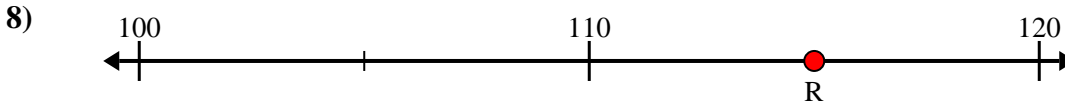

8. \_\_\_\_\_

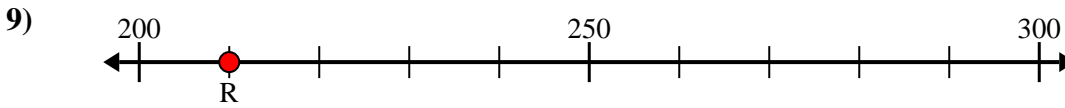











9. \_\_\_\_\_

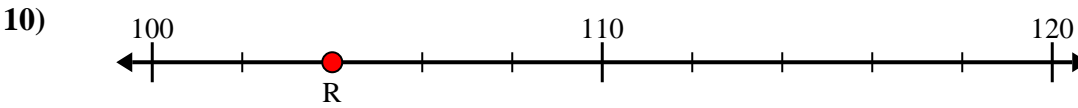

10. \_\_\_\_\_



Find the value of R.

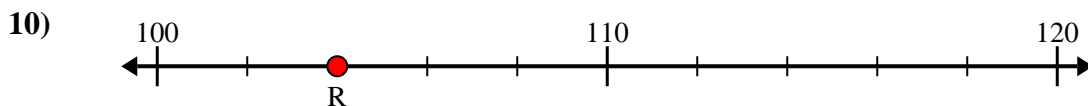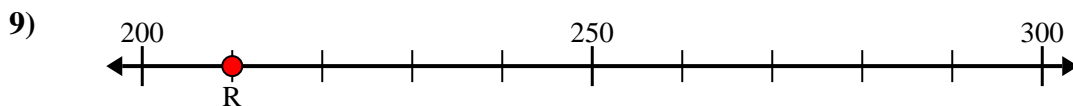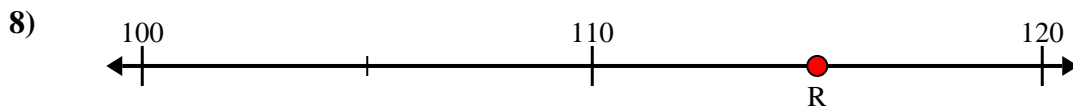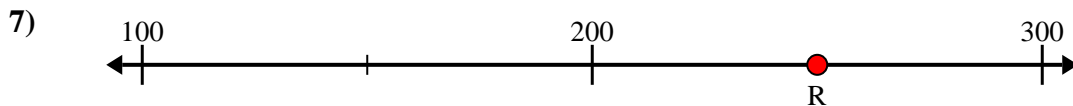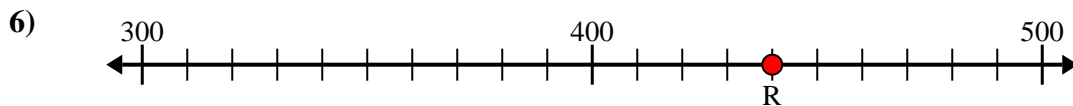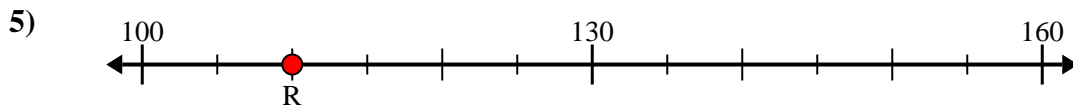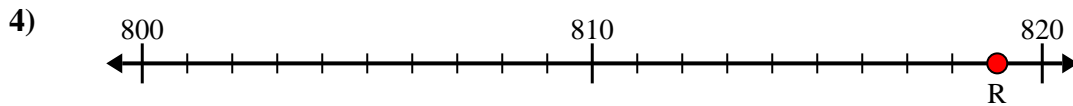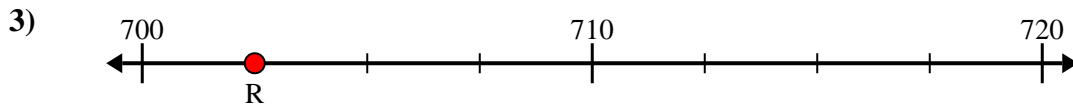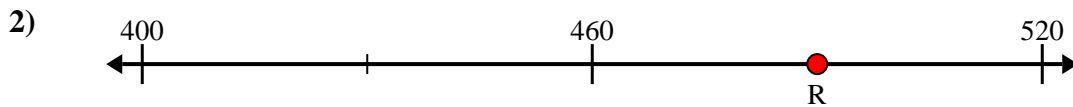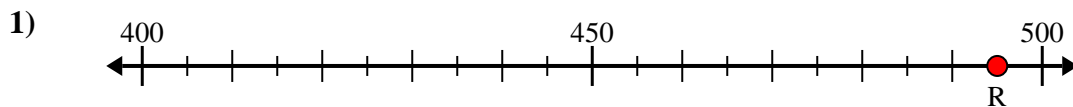

Answers

1. 495

2. 490

3. 702.5

4. 819

5. 110

6. 440

7. 250

8. 115


9. 210

10. 104




Find the value of R.


Answers

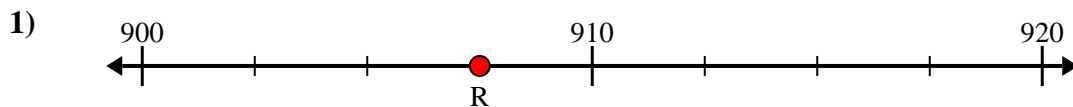


1. \_\_\_\_\_

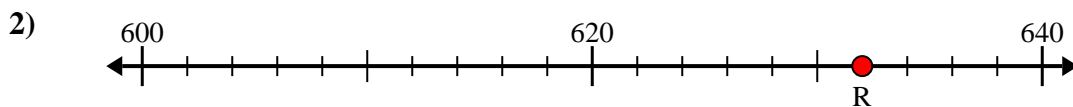


2. \_\_\_\_\_

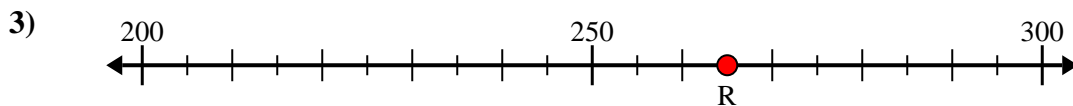


3. \_\_\_\_\_

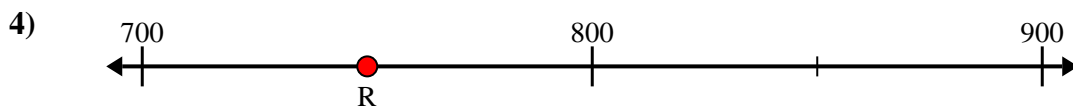


4. \_\_\_\_\_

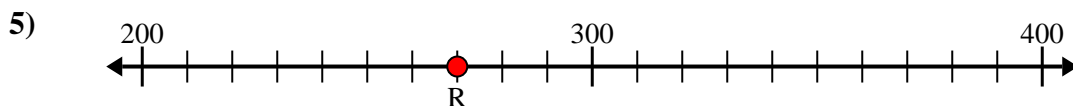


5. \_\_\_\_\_

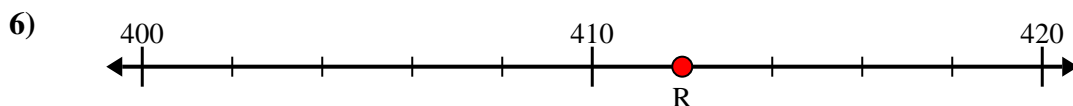


6. \_\_\_\_\_

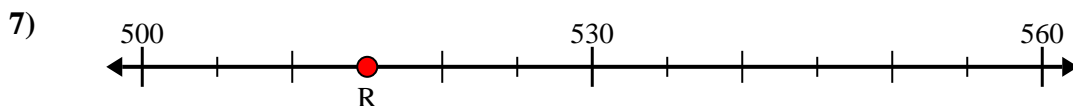


7. \_\_\_\_\_

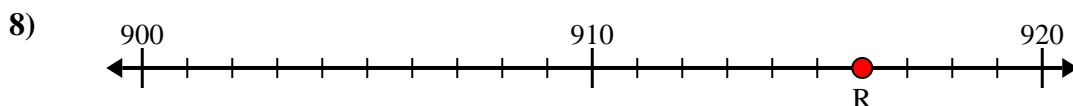

8. \_\_\_\_\_

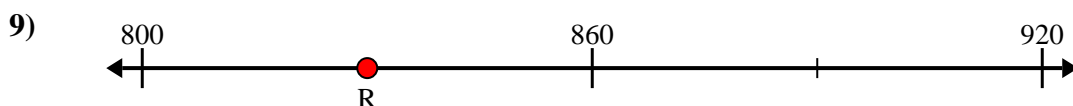











9. \_\_\_\_\_

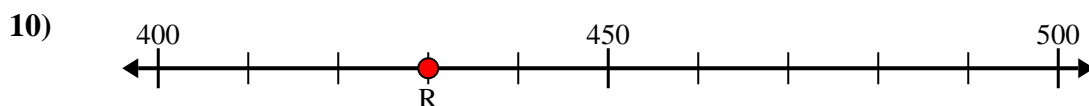

10. \_\_\_\_\_



Find the value of R.

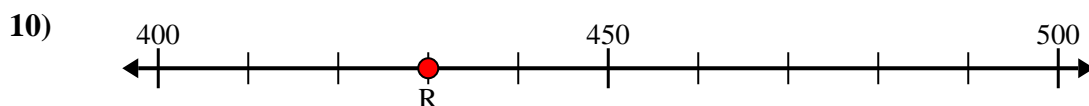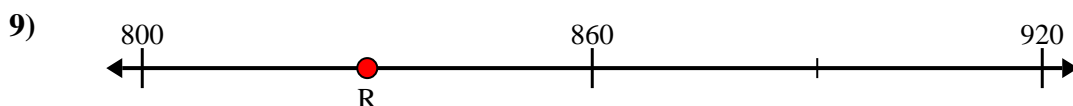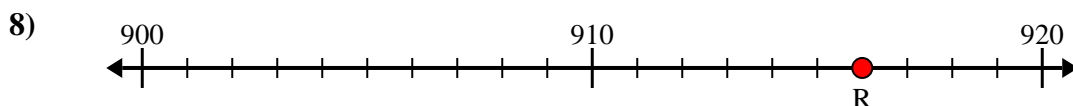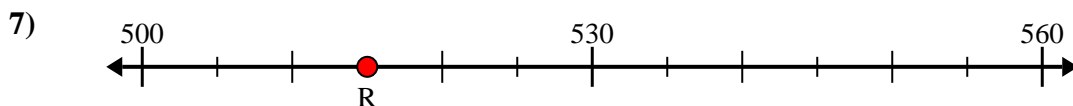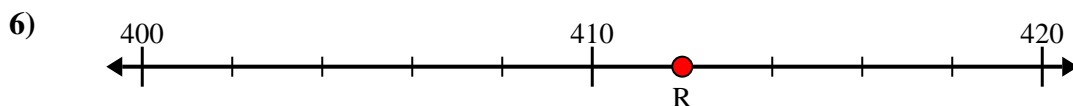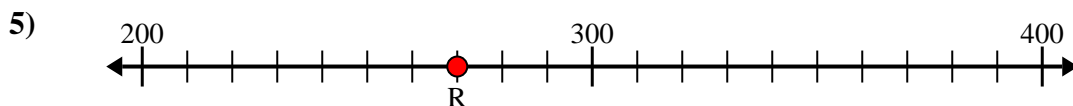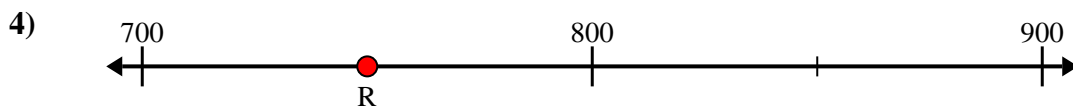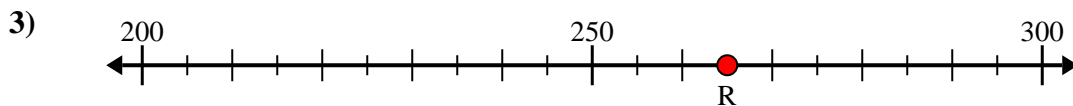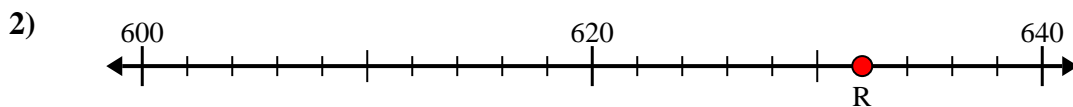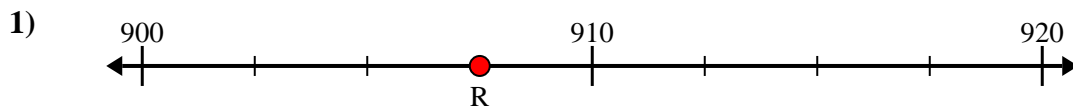

Answers

1. 907.5

2. 632

3. 265

4. 750

5. 270

6. 412

7. 515

8. 916


9. 830

10. 430




Find the value of R.


Answers

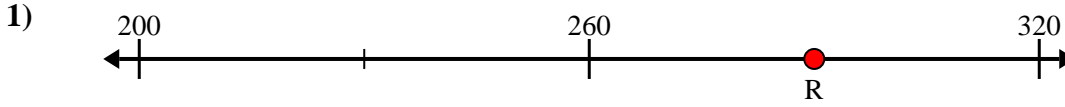

1. \_\_\_\_\_

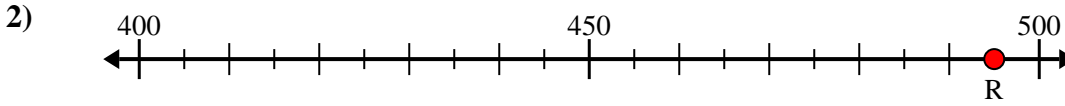


2. \_\_\_\_\_

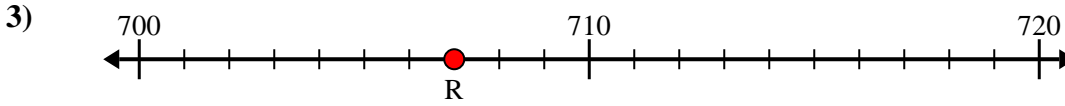


3. \_\_\_\_\_

4. \_\_\_\_\_

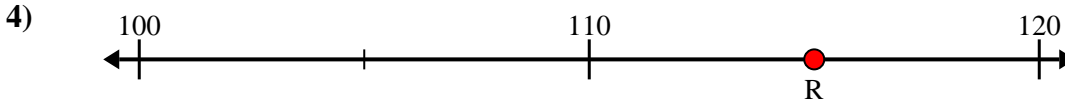


5. \_\_\_\_\_

6. \_\_\_\_\_

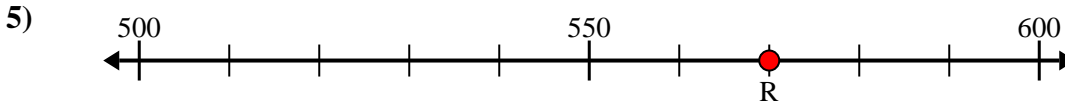





7. \_\_\_\_\_

8. \_\_\_\_\_

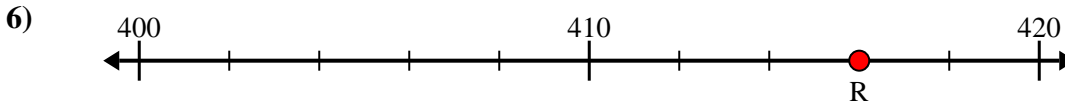











9. \_\_\_\_\_

10. \_\_\_\_\_

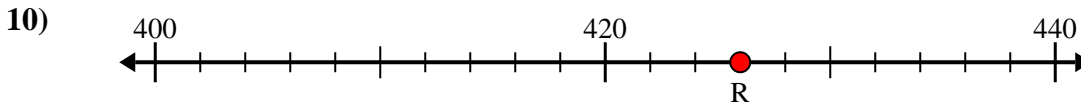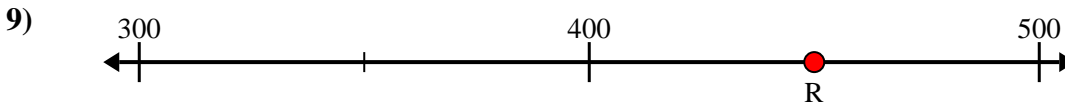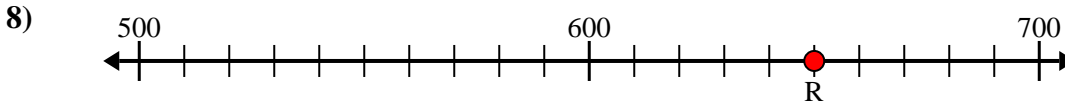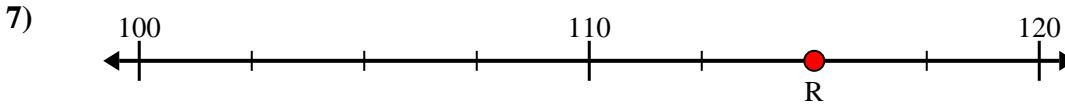



Find the value of R.

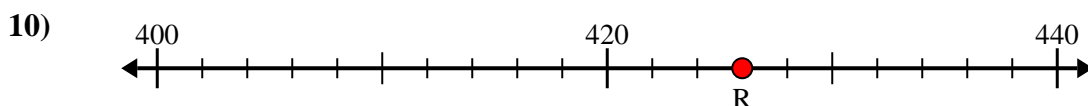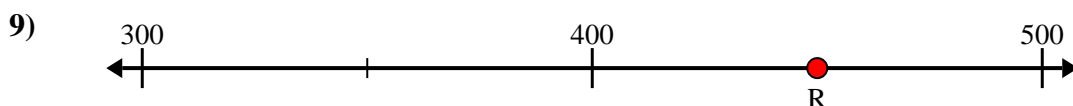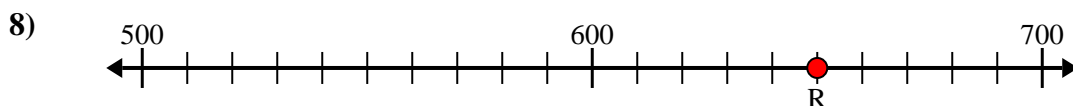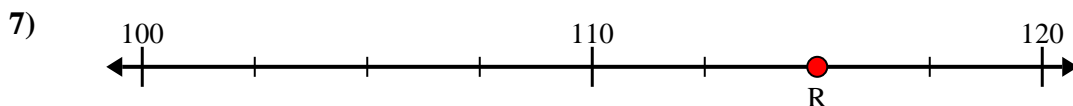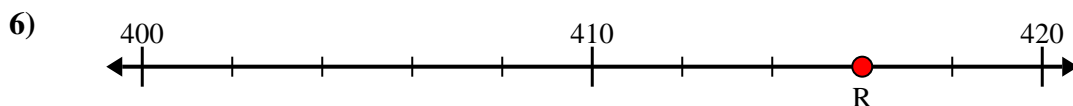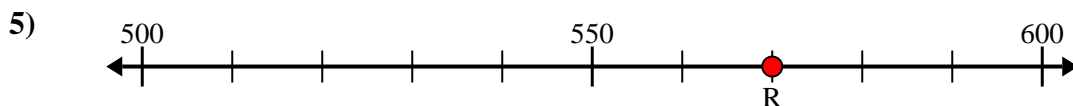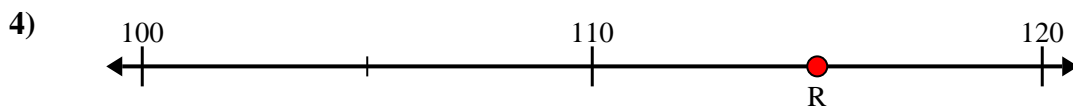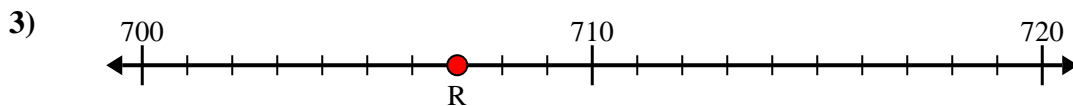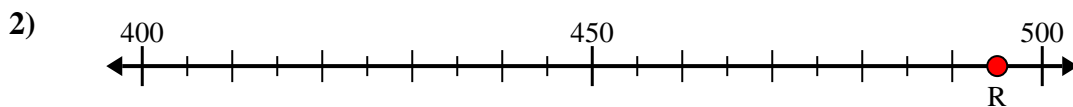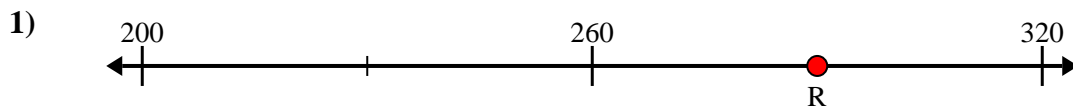

Answers

1. 290

2. 495

3. 707

4. 115

5. 570

6. 416

7. 115

8. 650

9. 450


10. 426






Find the value of R.


Answers

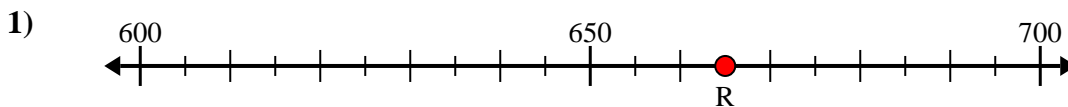


1. \_\_\_\_\_

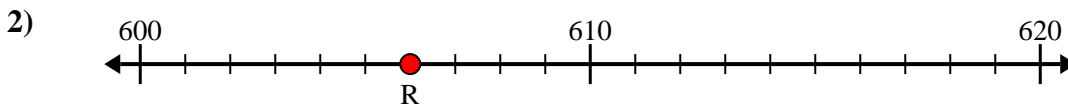


2. \_\_\_\_\_

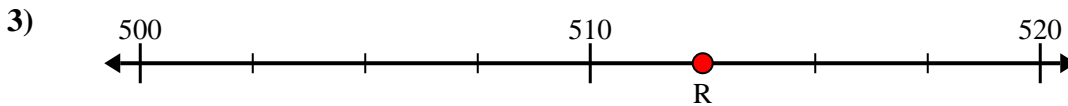


3. \_\_\_\_\_

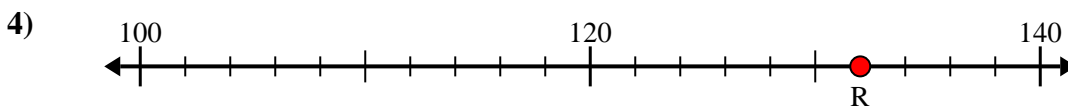


4. \_\_\_\_\_

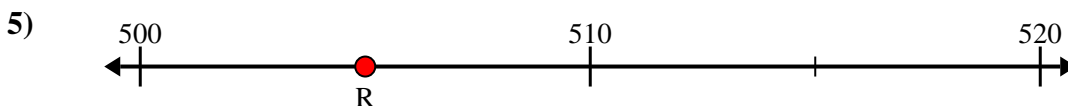


5. \_\_\_\_\_

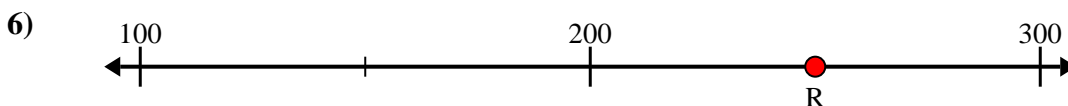


6. \_\_\_\_\_

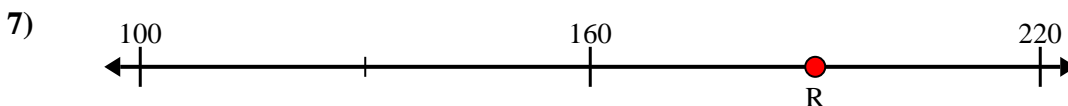


7. \_\_\_\_\_

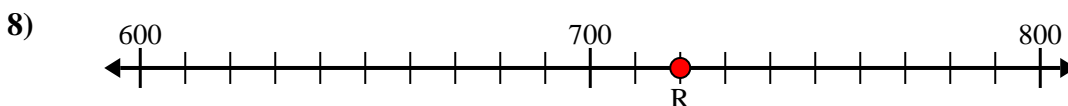

8. \_\_\_\_\_

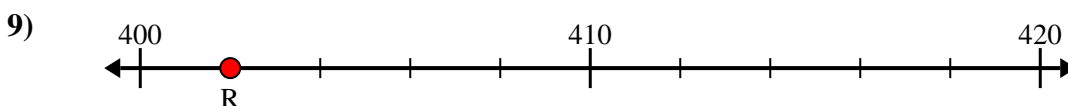











9. \_\_\_\_\_

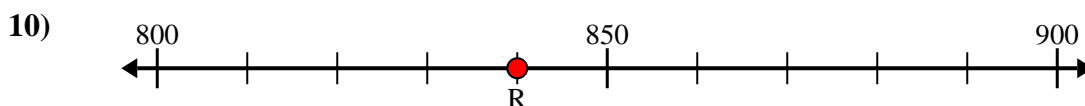

10. \_\_\_\_\_




Find the value of R.

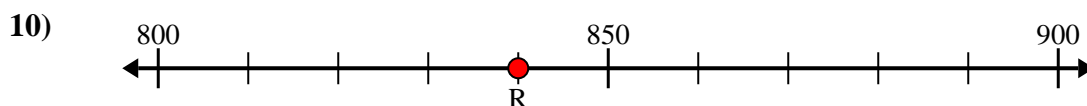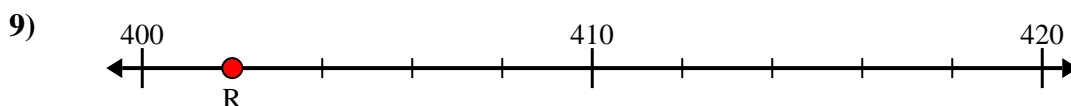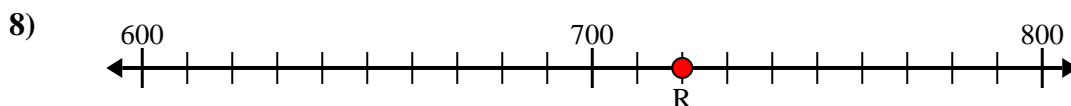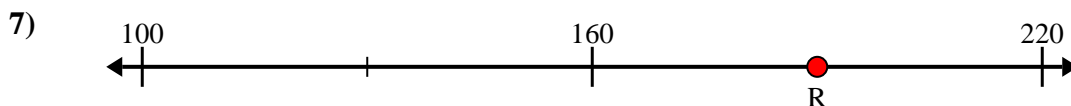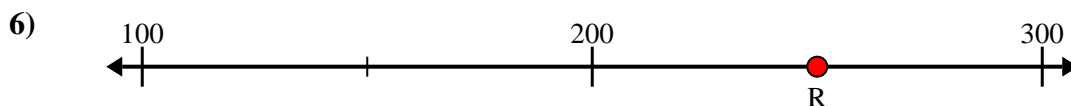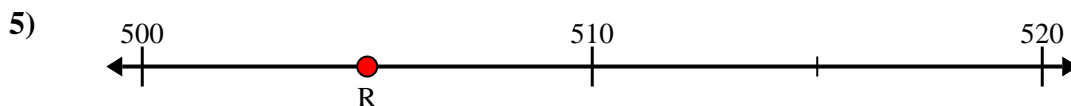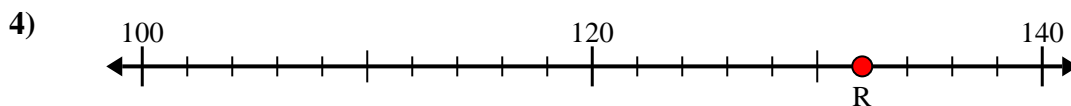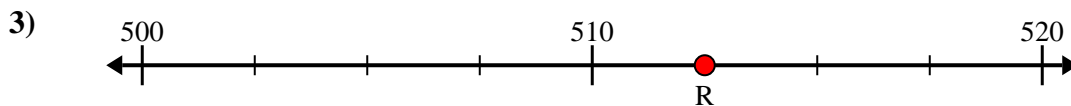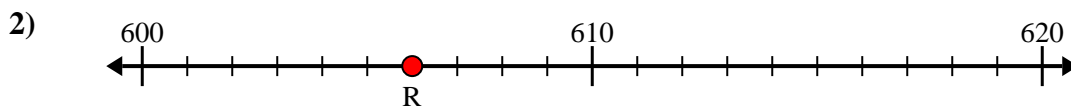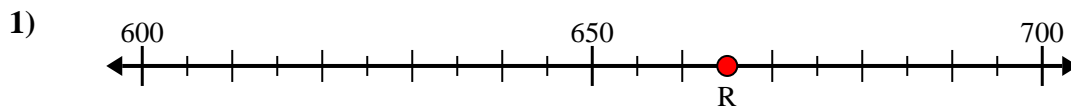Answers1. 6652. 6063. 512.54. 1325. 5056. 2507. 1908. 7209. 40210. 840




Find the value of R.


Answers

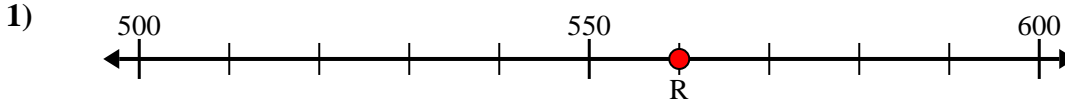


1. \_\_\_\_\_

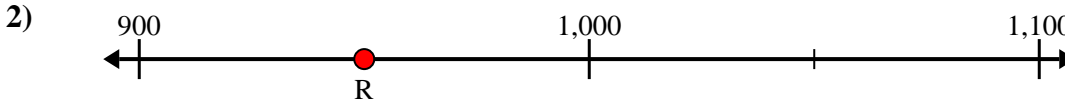


2. \_\_\_\_\_

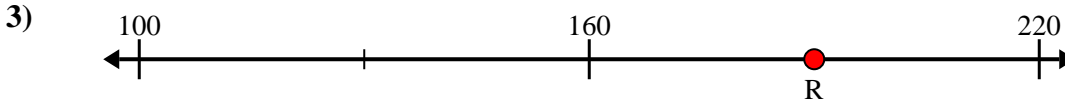


3. \_\_\_\_\_

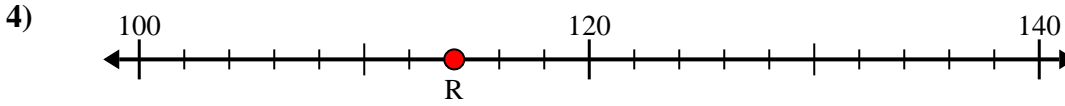


4. \_\_\_\_\_

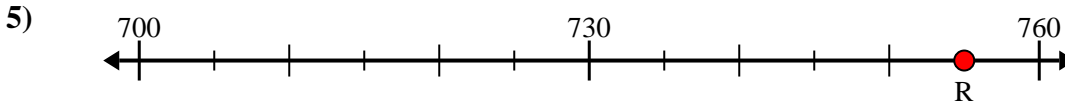


5. \_\_\_\_\_

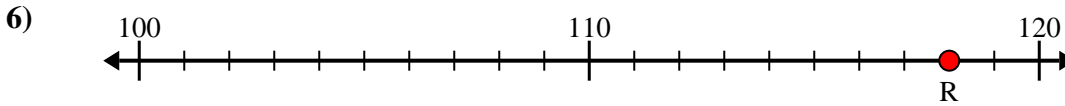


6. \_\_\_\_\_

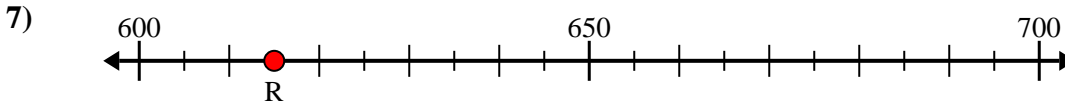


7. \_\_\_\_\_

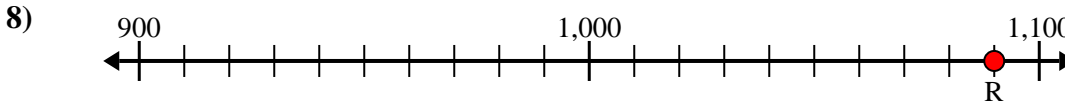

8. \_\_\_\_\_

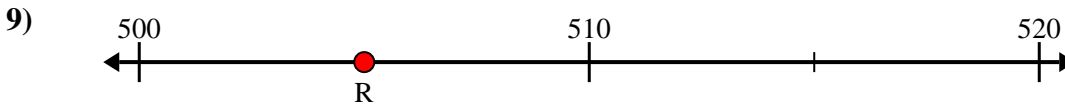











9. \_\_\_\_\_

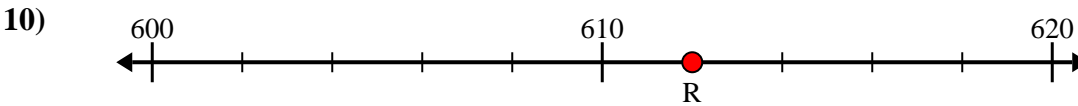

10. \_\_\_\_\_



Find the value of R.

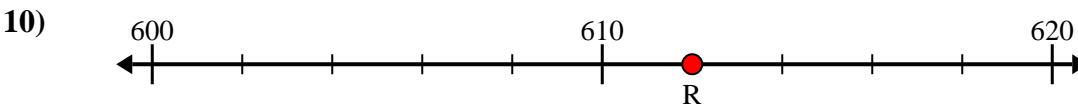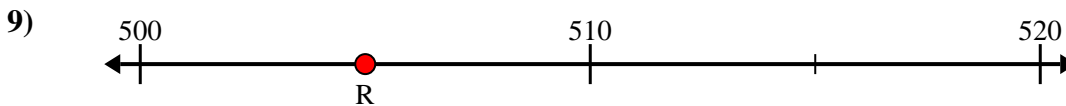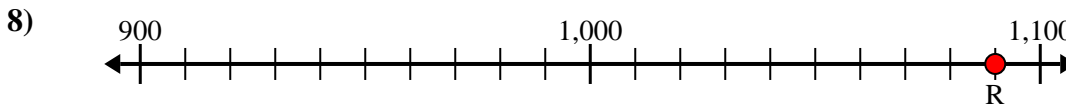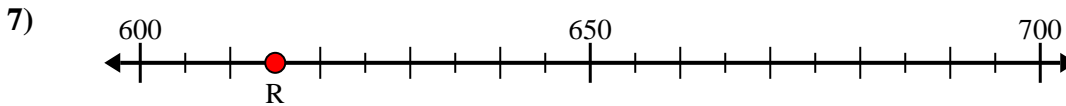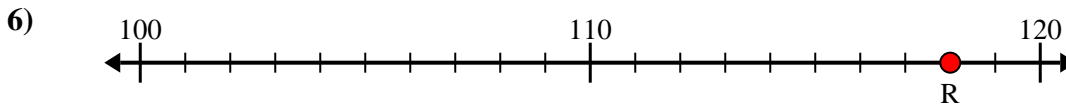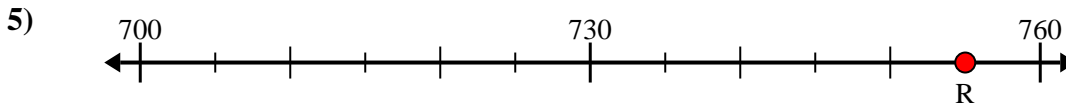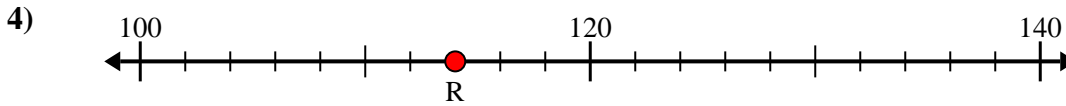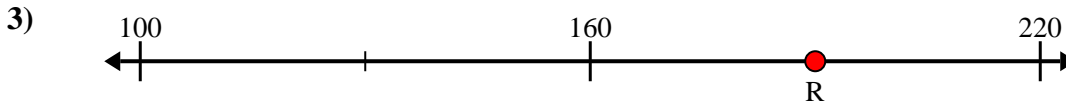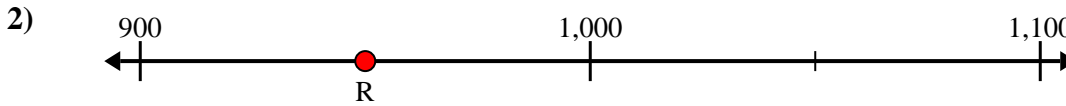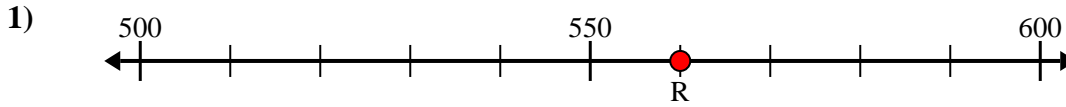

Answers

1. 560

2. 950

3. 190

4. 114

5. 755

6. 118

7. 615

8. 1,090


9. 505

10. 612




Find the value of R.


Answers

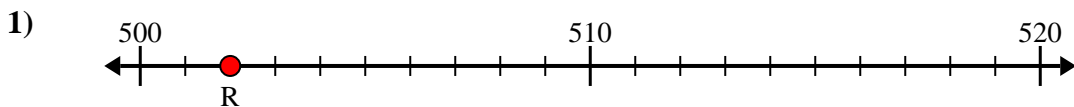


1. \_\_\_\_\_

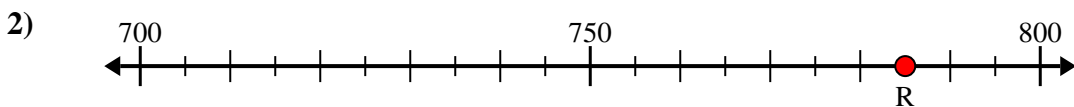


2. \_\_\_\_\_

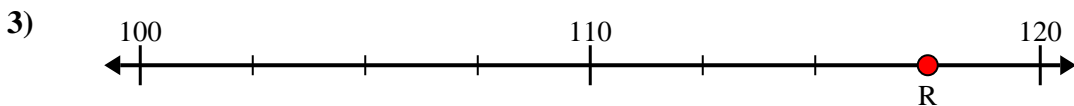


3. \_\_\_\_\_

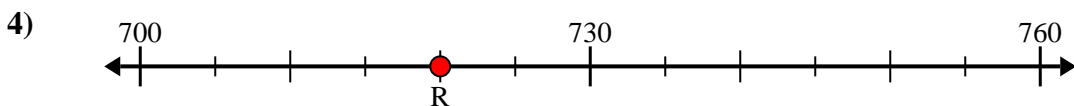


4. \_\_\_\_\_

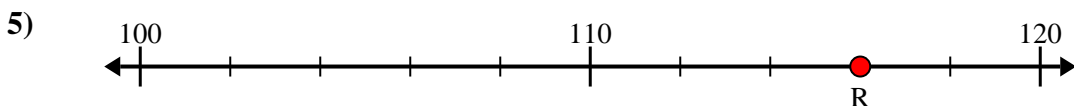


5. \_\_\_\_\_

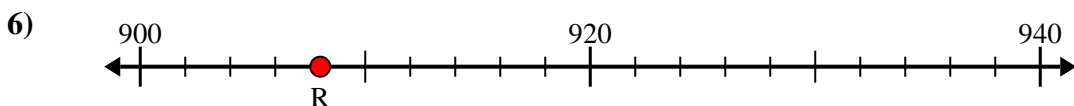


6. \_\_\_\_\_

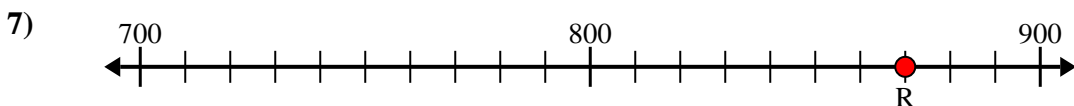


7. \_\_\_\_\_

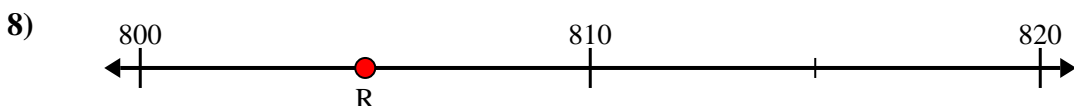

8. \_\_\_\_\_

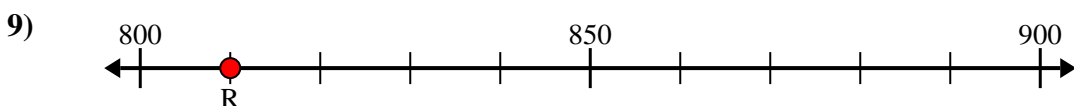











9. \_\_\_\_\_

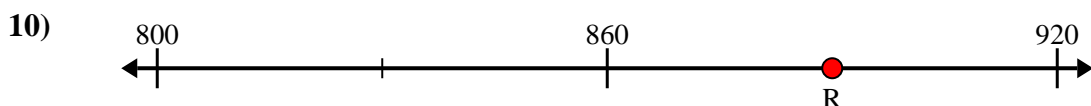

10. \_\_\_\_\_




Find the value of R.

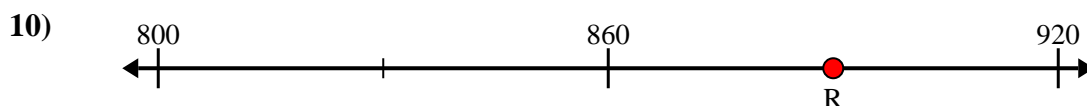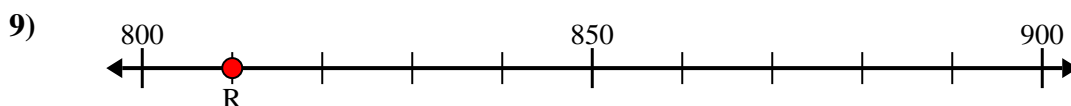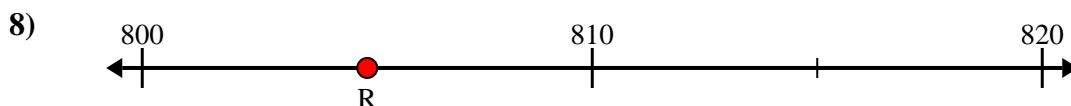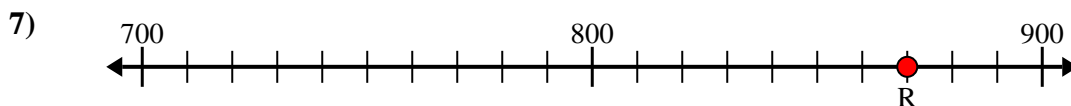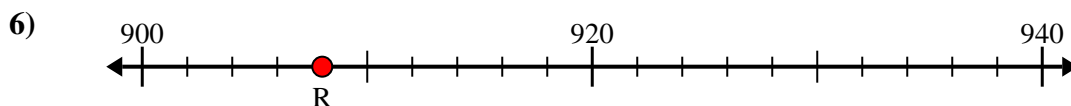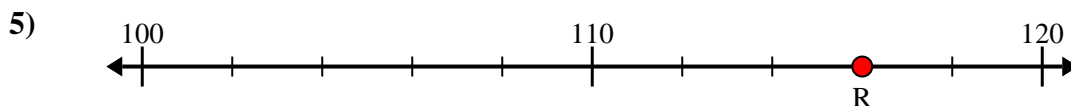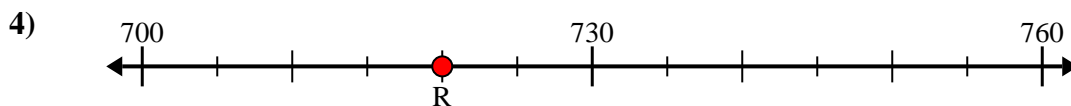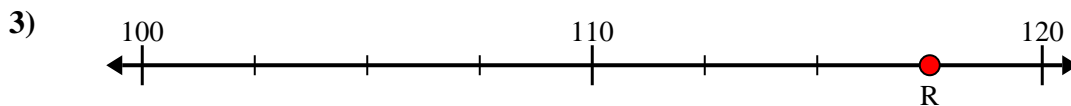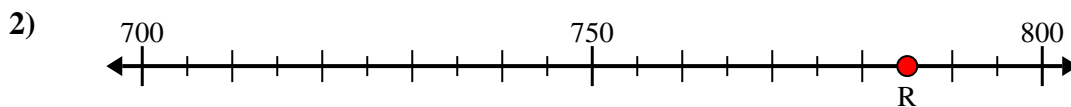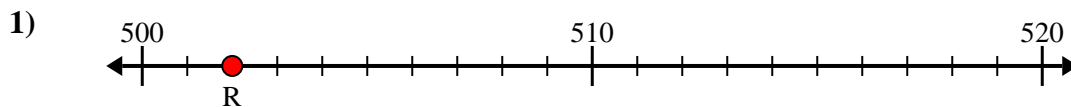**Answers**1. 5022. 7853. 117.54. 7205. 1166. 9087. 8708. 8059. 81010. 890




Find the value of R.


Answers

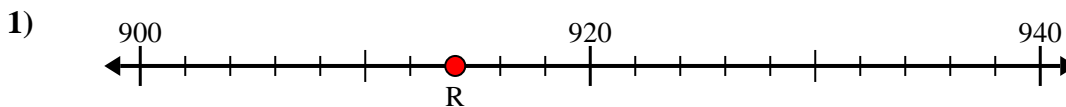


1. \_\_\_\_\_

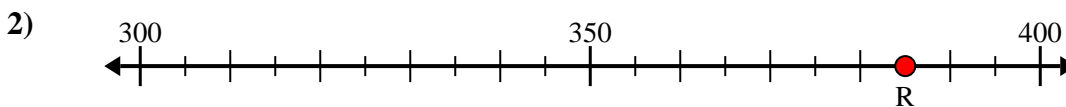


2. \_\_\_\_\_

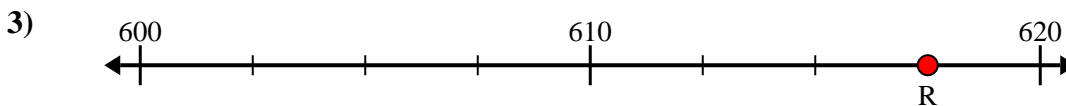


3. \_\_\_\_\_

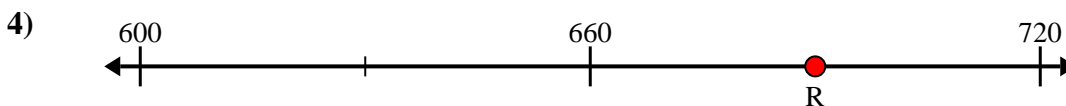


4. \_\_\_\_\_

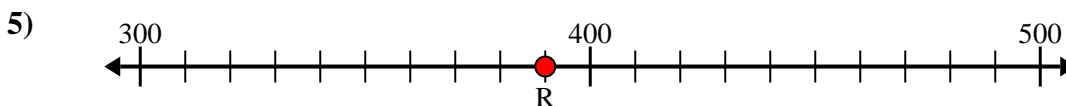


5. \_\_\_\_\_

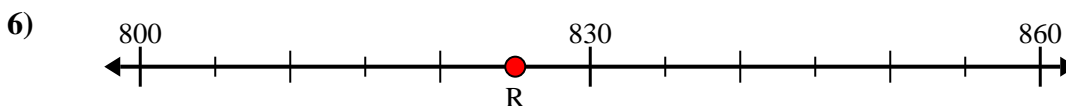


6. \_\_\_\_\_

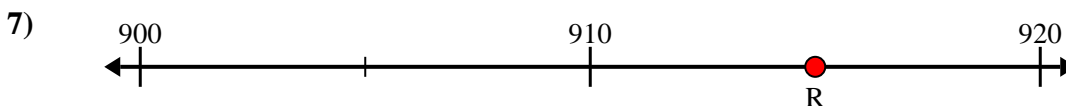


7. \_\_\_\_\_

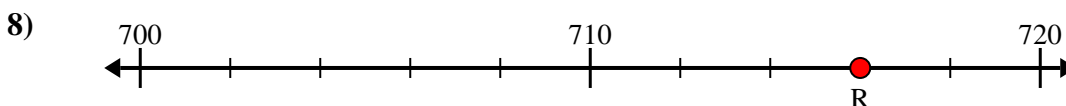

8. \_\_\_\_\_

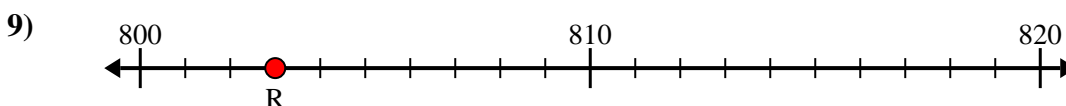











9. \_\_\_\_\_

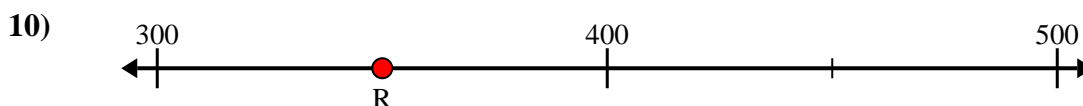

10. \_\_\_\_\_



Find the value of R.

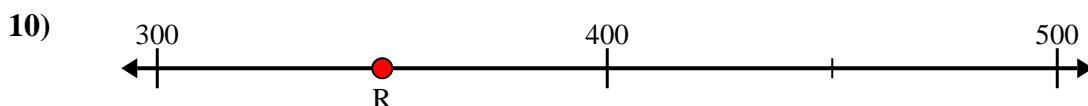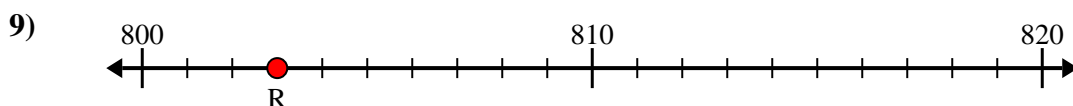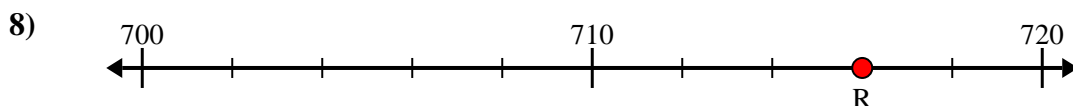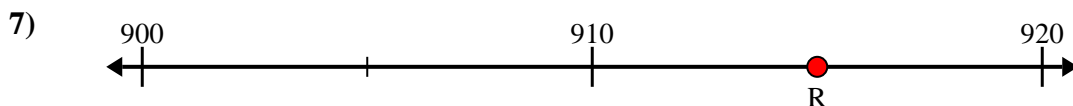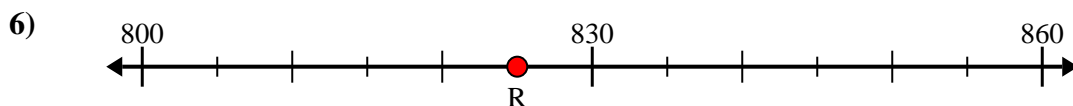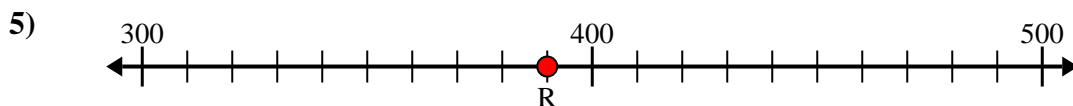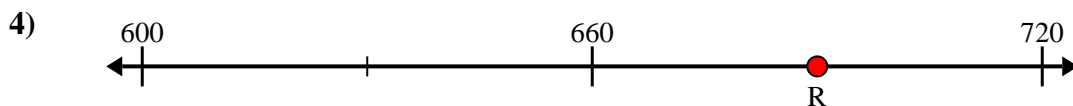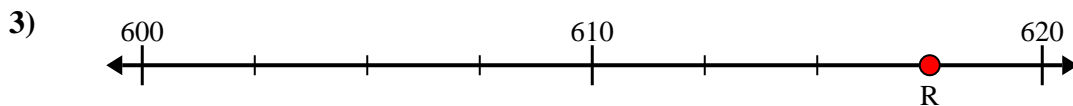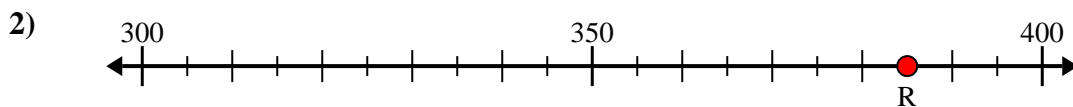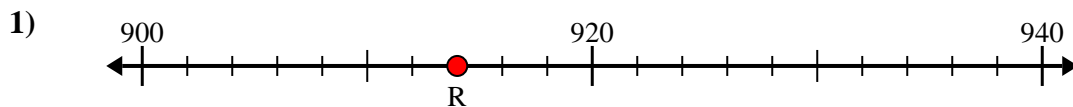

Answers

1. 914

2. 385

3. 617.5

4. 690

5. 390

6. 825

7. 915

8. 716

9. 803


10. 350






Find the value of R.


Answers

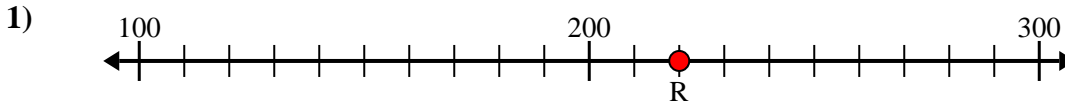


1. \_\_\_\_\_

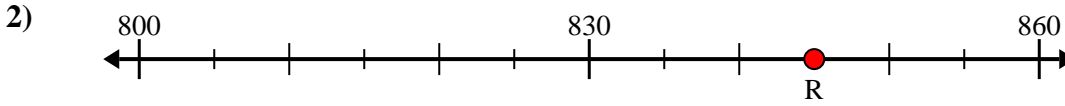


2. \_\_\_\_\_

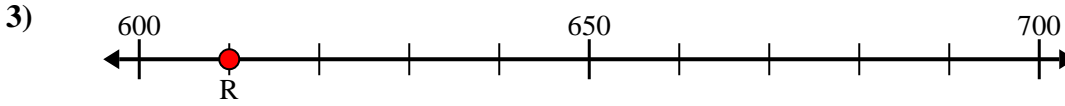


3. \_\_\_\_\_

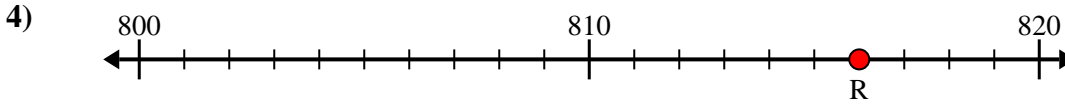


4. \_\_\_\_\_

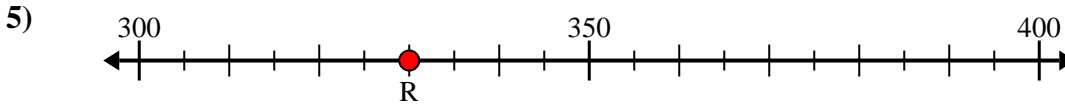


5. \_\_\_\_\_

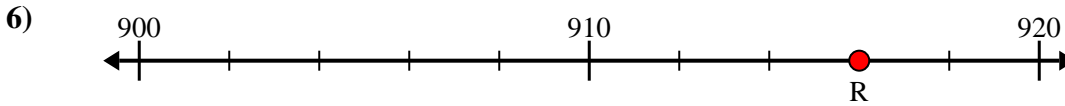


6. \_\_\_\_\_

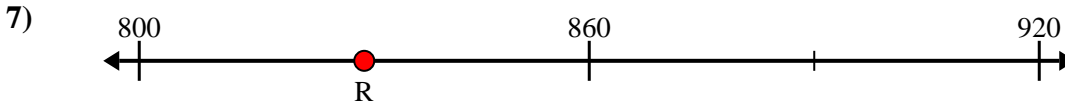


7. \_\_\_\_\_

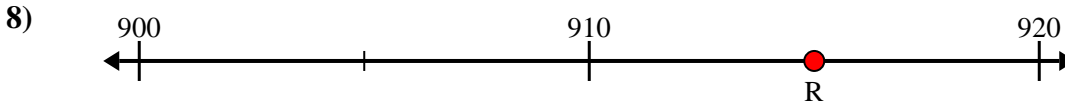

8. \_\_\_\_\_

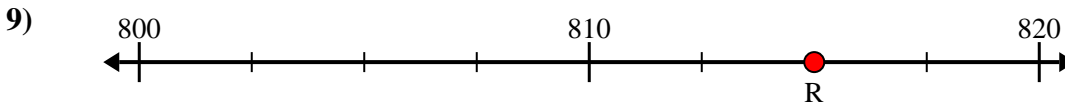











9. \_\_\_\_\_

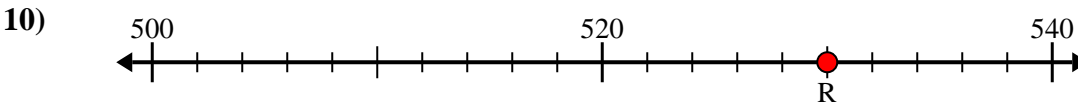

10. \_\_\_\_\_



Find the value of R.

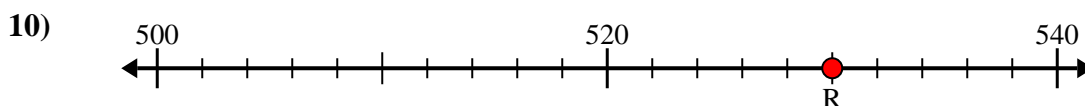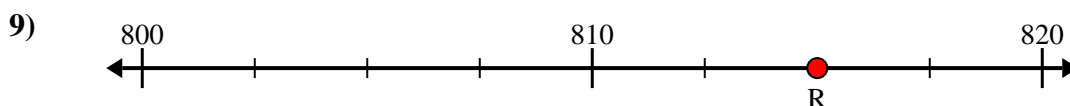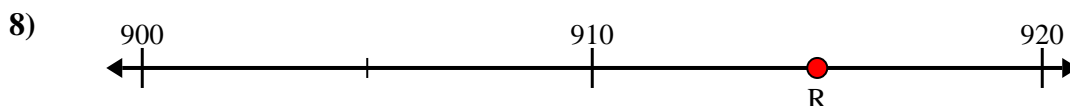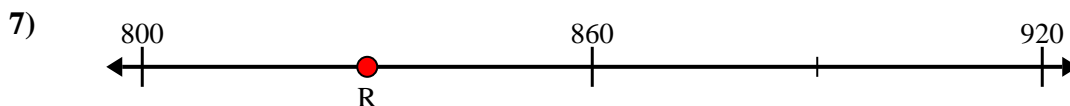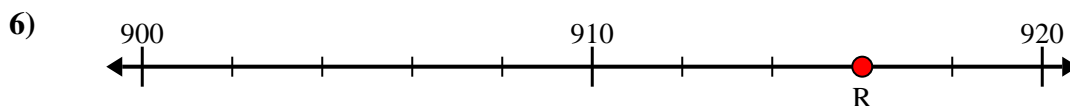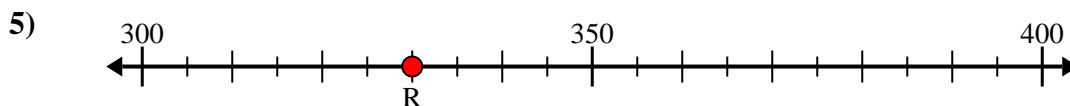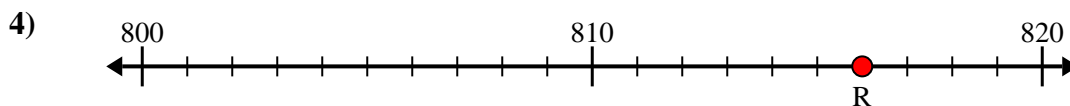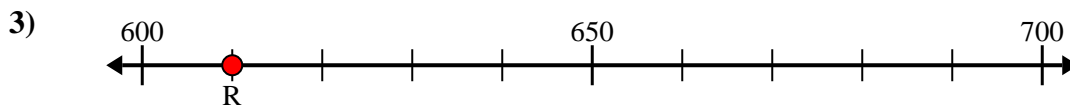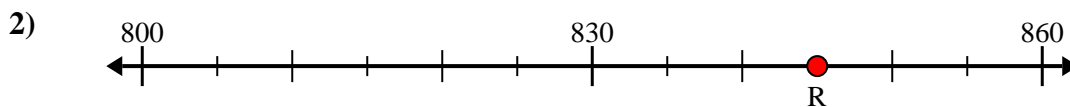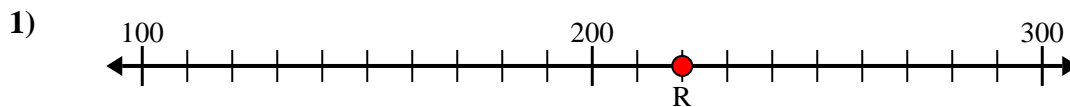

Answers

1. 220

2. 845

3. 610

4. 816

5. 330

6. 916

7. 830











8. 915

9. 815

10. 530



Find the value of R.

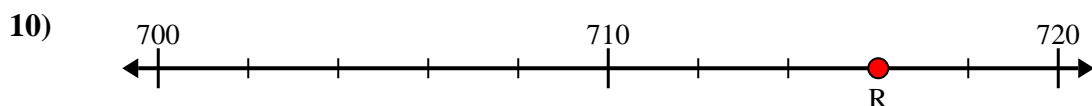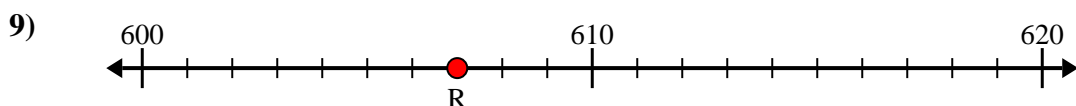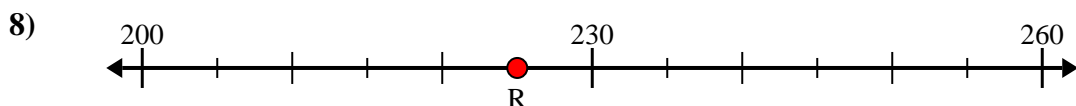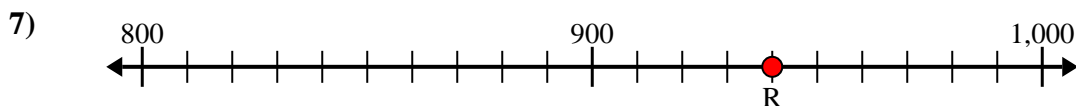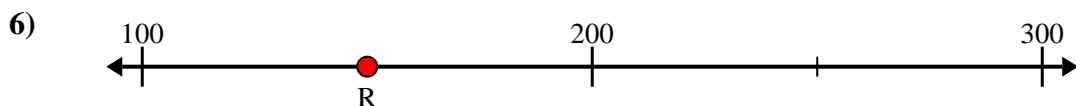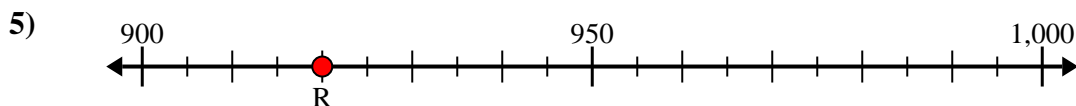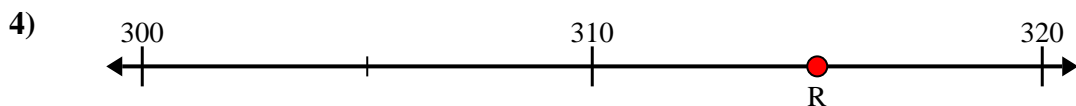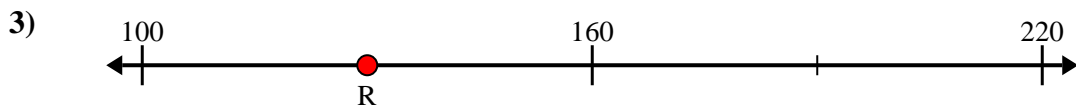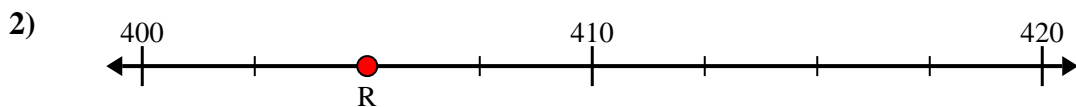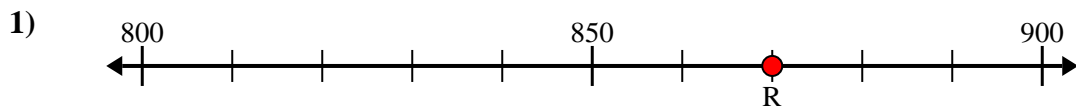

Answers

1. \_\_\_\_\_

2. \_\_\_\_\_

3. \_\_\_\_\_

4. \_\_\_\_\_

5. \_\_\_\_\_

6. \_\_\_\_\_

7. \_\_\_\_\_











8. \_\_\_\_\_

9. \_\_\_\_\_

10. \_\_\_\_\_



Find the value of R.

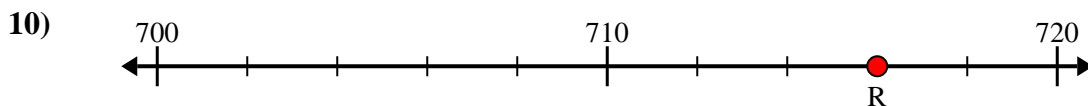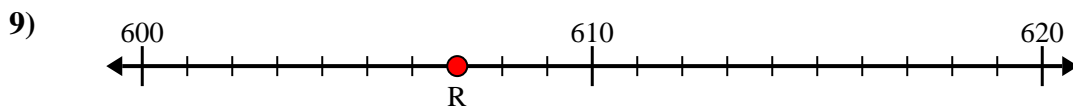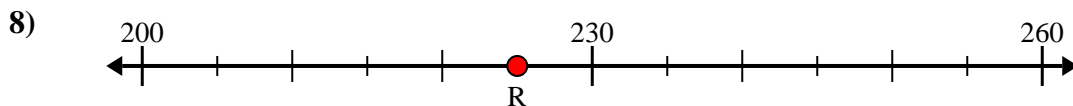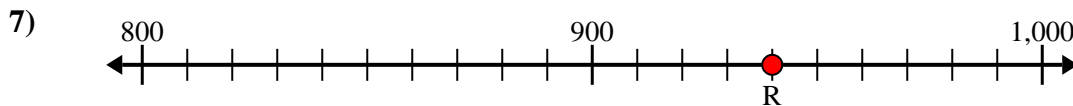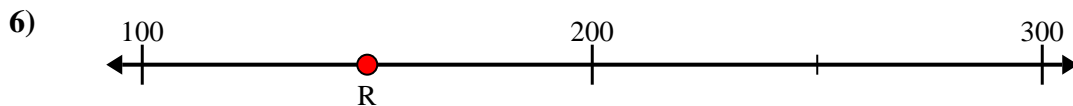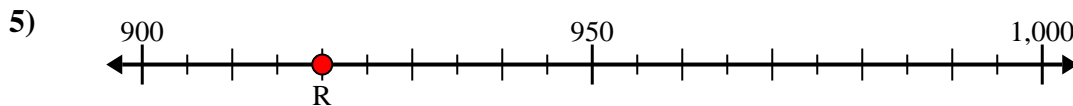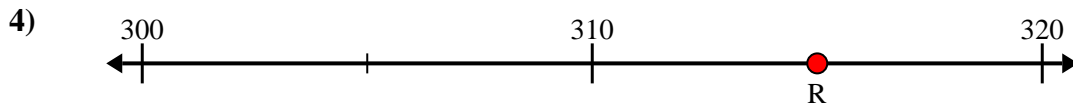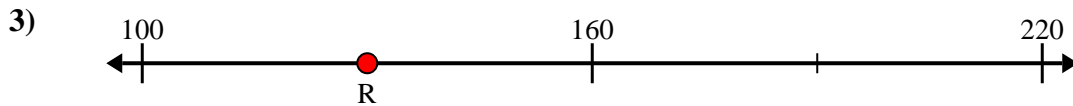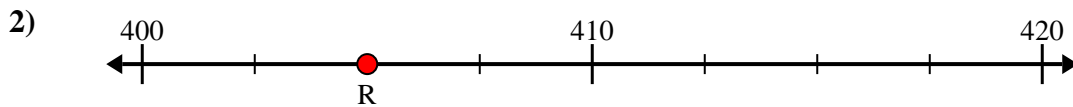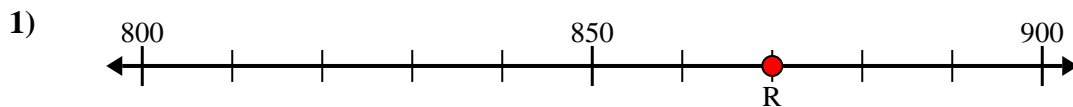

Answers

1. 870

2. 405

3. 130

4. 315

5. 920

6. 150

7. 940

8. 225

9. 607

10. 716